

ECE275 Final exam Fall 2022

Instructor: Vikas Dhiman (vikas.dhiman@maine.edu)

December 8, 2022

Student Name:

Student Email:

1 Instructions

- There are seven questions. First two questions (Prob 1 and Prob 2) are mandatory. **Do any four out of the five remaining problems.** For extra credit, do all seven.
- Maximum number of marks is 120 (140 with extra-credit). This exam amounts 10% toward the final grade.
- Time allowed is 120 minutes.
- In order to minimize distraction to your fellow students, you may not leave during the last 10 minutes of the examination.
- The examination is closed-book. One 8×11 in two-sided cheatsheet is allowed.
- Non-programmable calculators are permitted.
- Please use a pen or heavy pencil to ensure legibility. Colored pens/pencils are recommended for K-map grouping.
- Please show your work; where appropriate, marks will be awarded for proper and well-reasoned explanations.

Problem 1. A sequential circuit is to be used to control the operation of a vending machine which dispenses a \$0.25 product. The circuit has three inputs (N, D and Q) and two outputs (R and C). The coin detector mechanism in the vending machine is synchronized with the same clock as the sequential circuit you are to design. The coin detector outputs a single 1 to the N, D, or Q input for every nickel (5 cents), dime (10 cents), or quarter (25 cents), respectively, that the customer inserts. Only one input will be 1 at a time. When the customer has inserted at least \$0.25 in any combination of nickels, dimes, and quarters, the vending machine must give change and dispense the product. The coin return mechanism gives change by returning nickels to the customer. For every 1 output on C, the coin return mechanism will return one nickel to the customer. The product is dispensed when the circuit outputs a single 1 on output R. The circuit should reset after dispensing the product.

Example: The customer inserts a nickel, a dime, and a quarter. The circuit inputs and outputs could look like this:

Inputs: Money 0 0 0 5 5 5 5 15 15 15 40 35 30 25 25 0 0

Inputs	N=	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0
	D=	0	0	0	0	0	0	0	1	0	0	0	0	0	0	0	0	0
	Q=	0	0	0	0	0	0	0	0	0	0	1	0	0	0	0	0	0
	Outputs	R=	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0
	C=	0	0	0	0	0	0	0	0	0	0	0	1	1	1	0	0	0

Note that any number of 0's can occur between 1 inputs. Derive a Moore state table for the sequential circuit, and for each state indicate how much money the customer has inserted or how much change is due. (30 marks)

Moore state table

Money inserted	Change due	Present State PS	Next State			Output (R,C)	
			NDQ = 000	N (nickel) 100	D (dime) 010		Q (quarter) 001
0	0	S ₀	S ₀	S ₁	S ₂	S ₃	0 0
5	0	S ₁	S ₁	S ₂	S ₄	S ₅	0 0
10	0	S ₂	S ₂	S ₄	S ₆	S ₇	0 0
25	0	S ₃	S ₀	S ₀	S ₀	S ₀	1 0
15	0	S ₄	S ₄	S ₆	S ₃	S ₈	0 0
30	5	S ₅	S ₃	S ₃	S ₃	S ₃	0 1
20	0	S ₆	S ₆	S ₃	S ₅	S ₉	0 0
35	10	S ₇	S ₅	S ₅	S ₅	S ₅	0 1
40	15	S ₈	S ₇	S ₇	S ₇	S ₇	0 1
45	20	S ₉	S ₈	S ₈	S ₈	S ₈	0 1

0 0000
 ⋮ ⋮
 9 1001

Problem 2. Realize a BCD to excess-3 code converter using a 4-to-16 decoder with active low outputs and a minimum number of gates. (The excess-3 code is obtained from the binary numbers (0-9) by adding 3 (0011) to each of the binary numbers.) (Active low outputs mean that the selected output pin is 0, while all others are 1.) (10 marks)

$$Y_3 = \overline{D_5} \cdot \overline{D_6} \cdot \overline{D_7} \cdot \overline{D_8} \cdot \overline{D_9}$$




$$Y_2 = D_5 + D_6 + D_7 + D_8 + D_9$$

Count
 0
 1
 2
 3
 4
 5
 6
 7
 8
 9

	B	C	D
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0
9	0	0	1

Excess-3

	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	1	1
1	0	1	0	0
2	0	1	0	1
3	0	1	1	0
4	0	1	1	1
5	1	0	0	0
6	1	0	0	1
7	1	0	1	0
8	1	0	1	1
9	1	1	0	0

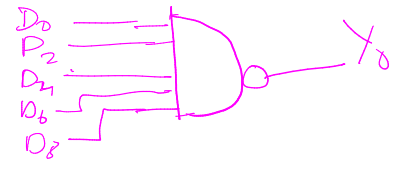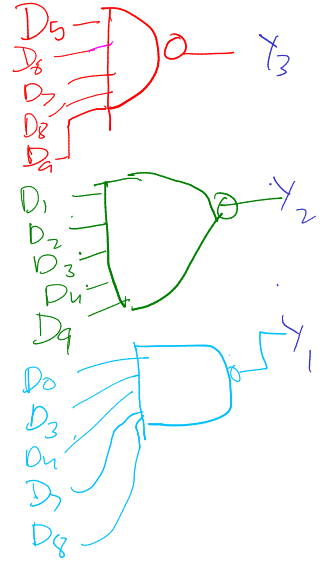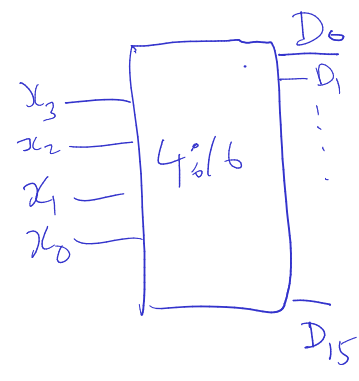

20mm x 2
40mm

Problem 3. Reduce the following state table to a minimum number of states using implication charts (20 marks).

Present State	Next State		Output
	X = 0	1	Z
A	A	B	1
B	C	E	0
C	F	G	1
D	C	A	0
E	B	G	1
F	F	H	1
G	C	F	0
H	F	B	1
I	C	E	0

X due to output difference

X due to Round 1

X due to Round 2

X due to Round 3

X due to Round 4

A									
B	X								
C	A=F B=G	X							
D		E=A	X						
E	A=I B=G		D=I	X					
F	A=H B=I		F=H G=I	X	E=H G=I				
G		E=F		A=E	X	X			
H	A=F		G=B	X	E=F G=B	H=F I=B	X		
I		C=E C=E		A=E	X	X	E=E	X	
	A	B	C	D	E	F	G	H	I

$$\underbrace{B \equiv I}_B$$

$$\underbrace{F \equiv H}_F$$

Problem 4. 1. For the following state table, use the three guidelines to determine which of the three possible nonequivalent state assignments should give the best solution (20 marks).

(40 min)

2. Using your answer to (a), derive J-K flip-flop input equations and the output equations (20 marks).

x2
(80 min)

Present State	Next state				Outputs Z_1, Z_2			
	$X_1, X_2 = 00$	01	11	10	$X_1, X_2 = 00$	01	11	10
A	A	A	C	C	01	01	01	01
B	B	D	B	D	11	11	11	11
C	A	A	B	D	11	11	00	00
D	D	B	A	C	01	01	01	01

Guidelines


Highest priority: $\alpha \rightarrow \beta$: $(A, C)^z, (B, C)^z, (A, D)^z$

Medium priority: $\alpha \rightarrow \beta$: $(A, C), (B, D), (A, B, D), (A, B, C, D)$

Lowest priority: $\alpha \rightarrow \beta$: $00/01 (A, D), 00/11 (B, C)$

4 states . 2 ff
 $2^1 < 4 \leq 2^2$

State map

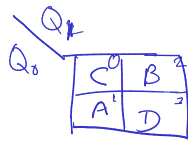

State	State assignment Q_1, Q_0
A	01
B	10
C	00
D	11

Present State	Next state				Outputs Z_1, Z_2			
	$X_1, X_2 = 00$	01	11	10	$X_1, X_2 = 00$	01	11	10
A	A	A	C	C	01	01	01	01
B	B	D	B	D	11	11	11	11
C	A	A	B	D	11	11	00	00
D	D	B	A	C	01	01	01	01

PS	Q_1, Q_0	NS				Outputs (Z_1, Z_2)			
		$X_1, X_2 = 00$	01	11	10	$X_1, X_2 = 00$	01	11	10
C	00	01	01	10	11	11	11	00	00
A	01	01	01	00	00	01	01	01	01
D	11	11	10	01	00	01	01	01	01
B	10	10	11	10	11	11	11	11	11

Q_1^+, Q_0^+	X_1, X_0	01	11	10
00	0	0	1	1
01	0	0	0	0
11	1	1	0	0
10	1	1	1	1

Q_1^+, Q_0^+	X_1, X_0	01	11	10
00	0	0	1	1
01	0	0	0	0
11	1	d	d	d
10	1	d	d	d

$J_1 = X_1 \overline{Q_0}$

Q_1^+, Q_0^+	X_1, X_0	01	11	10
00	0	d	d	d
01	0	d	d	d
11	1	0	0	1
10	1	0	0	0

$K_1 = X_1 Q_0$

JK excitation

Q_1	Q_1^+	J_1	K_1
0	0	0	d
0	1	1	d
1	0	d	0
1	1	d	0

Q_0

	$x_1 x_2$	00	01	11	10
Q_1	00	1	1	0	1
	01	1	1	0	0
	11	1	0	1	0
	10	0	1	0	1

Q_0

J_0

	$x_1 x_2$	00	01	11	10
Q_1	00	1	1	0	1
	01	d	d	d	d
	11	d	d	d	d
	10	0	1	0	1

Q_0

K_0

	$x_1 x_2$	00	01	11	10
Q_1	00	d	d	d	d
	01	0	0	1	1
	11	0	1	0	1
	10	d	d	d	d

Q_0

$$J_0 = x_1 \bar{x}_2 + \bar{x}_1 x_2 + \bar{x}_1 \bar{Q}_1$$

$$\bar{J}_0 = x_1 x_2 + \bar{x}_1 \bar{x}_2 Q_1$$

$$J_0 = (\bar{x}_1 + \bar{x}_2) (x_1 + x_2 + \bar{Q}_1)$$

$$K_0 = x_1 \bar{Q}_1 + x_1 \bar{x}_2 + \bar{x}_1 x_2 Q_1$$

Q_0	K_0
0	d
1	Q_1^+

Z_1

	$x_1 x_2$	00	01	11	10
Q_1	00	1	1	0	0
	01	0	0	0	0
	11	0	0	0	0
	10	1	1	1	1

Q_0

Q_0	J_0
0	Q_0^+
1	d

Z_2

	$x_1 x_2$	00	01	11	10
Q_1	00	1	1	0	0
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1


Q_0

$$Z_1 = Q_1 \bar{Q}_0 + \bar{x}_1 \bar{Q}_0$$

$$Z_2 = \bar{x}_1 + Q_0 + Q_1$$

Problem 5. Use a 4-to-1 multiplexer and a minimum number of external gates to realize the function $F(w, x, y, z) = \sum m(3, 4, 5, 7, 10, 14) + \sum d(1, 6, 15)$. The inputs are only available uncomplemented (20 marks).



$\bar{w}, \bar{x}, \bar{y}, \bar{z}$

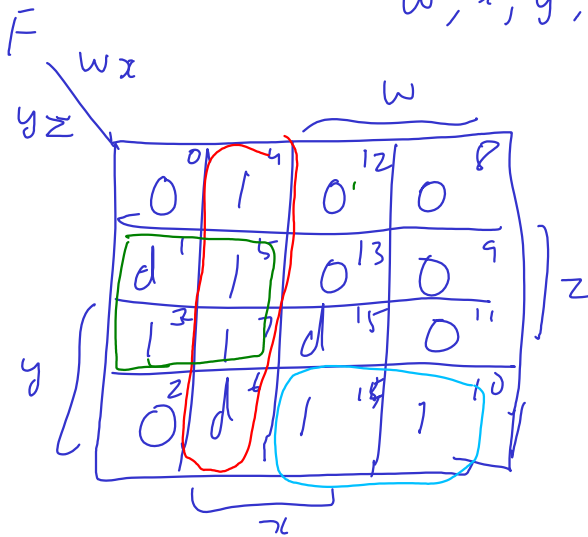

$$F = \bar{w}x + \bar{w}z + wy\bar{z}$$

w occurs 3 times
 x occurs 1 times
 y " 1 "
 z " 2 times

Pick w, z as select bits

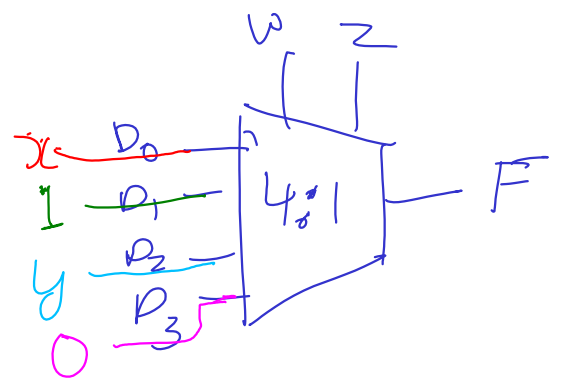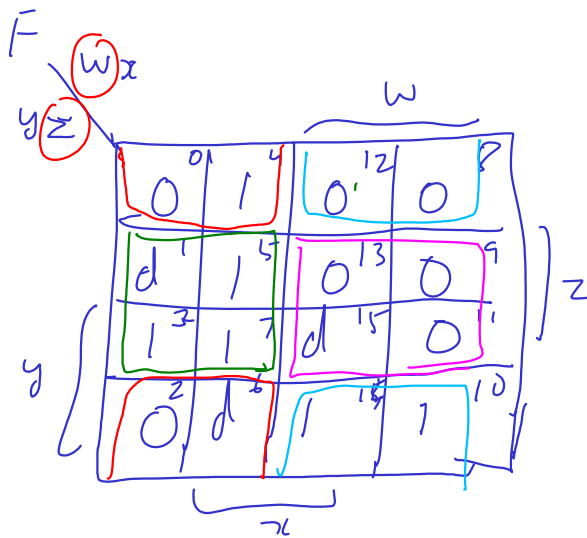

when wz = 00

$$F = D_0 = ?$$



$$F = D_0 = x$$


when wz = 01

$$F = D_1 = ?$$

$$F = D_1 = 1$$

when wz = 10

$$F = D_2 = ?$$

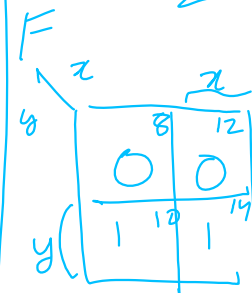


$$F = D_2 = y$$

when wz = 11

$$F = D_3 = ?$$

$$F = D_3 = 0$$

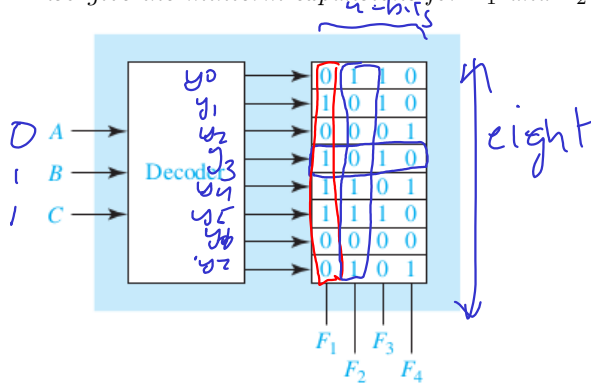Problem 6. The following diagram shows the pattern of 0's and 1's stored in a ROM with eight words and four bits per word. What will be the values of $F_1, F_2, F_3,$ and F_4 if $A = 0$ and $B = C = 1$? Also give the minterm expansions for F_1 and F_2 (20 marks).



A	B	C	y_0	y_1	y_2	y_3	y_7
0	0	0	1	0	...	0	0
0	0	1	0	1	...	0	0
0	1	1	0	0	1	0	0

when $ABC = 011$

then $F_1 F_2 F_3 F_4 = 1010$

$$\left\{ \begin{array}{l} F_1 = 1 \\ F_2 = 0 \\ F_3 = 1 \\ F_4 = 0 \end{array} \right.$$

minterm expansion for F_1

Recall $y_0 = \bar{A}\bar{B}\bar{C} = m_0$


for a decoder $y_1 = \bar{A}\bar{B}C = m_1$

$$F_1 = m_1 + m_3 + m_4 + m_5 = \sum m(1, 3, 4, 5)$$

$$F_2 = m_0 + m_4 + m_5 + m_7 = \sum m(0, 4, 5, 7)$$

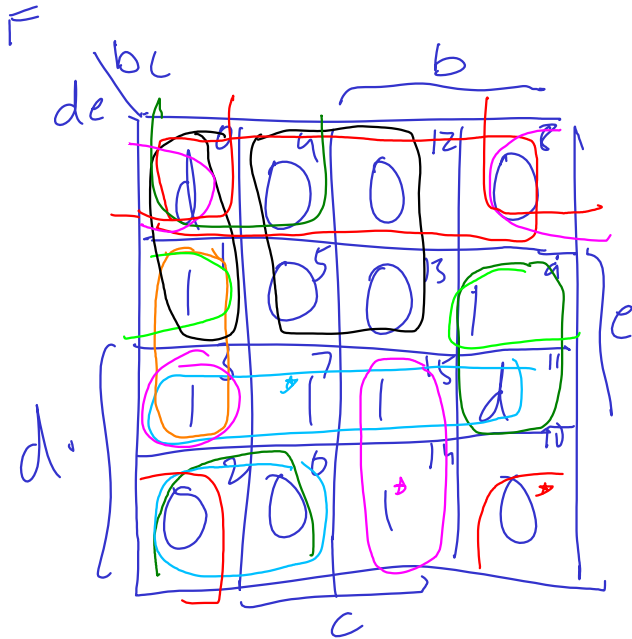
Problem 7. Find the minimum cost circuit for the following function using K-map. Find both ~~sum-of-products and product-of-sum forms~~ and find the minimum cost one.

$$F(a, b, c, d, e) = \prod M(2, 4, 5, 6, 8, 10, 12, 13, 16, 17, 18, 22, 23, 24) + \prod D(0, 11, 30, 31) \quad (20 \text{ marks}).$$



$$a=0$$

$$\bar{a}=1$$

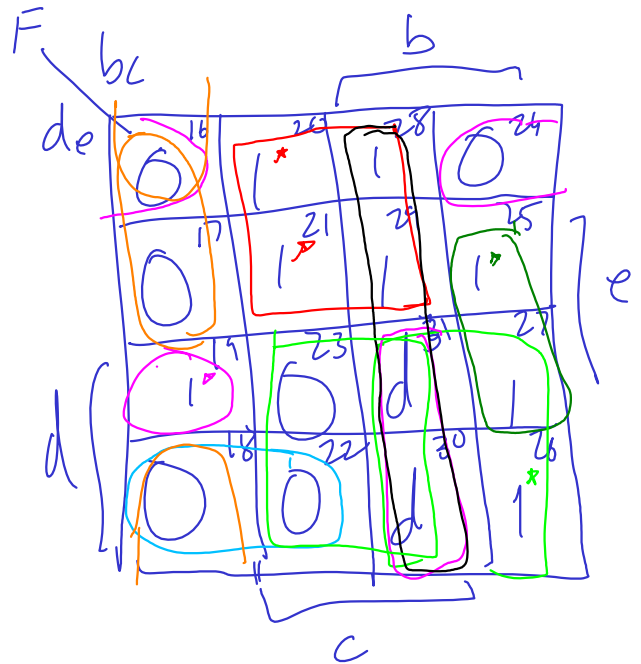

$$a=1$$

At Maxterms $F=0$

SOP form

$$F = bcd + \bar{a}de + \bar{a}\bar{c}\bar{d}\bar{e} + b\bar{c}e + ac\bar{d} + \bar{b}\bar{c}de + abd$$

$$\text{Cost} = 7 + 1 + 3 \times 5 + 4 \times 2 + 7 = 38$$

POS form



$$\bar{F} = \bar{a}\bar{c}\bar{e} + \bar{a}c\bar{d} + \bar{b}d\bar{e} + acd + \bar{c}\bar{d}\bar{e} + a\bar{b}\bar{c}\bar{d}$$

$$F = (a+c+e)(a+\bar{c}+d)(b+\bar{d}+e)(\bar{a}+\bar{c}+\bar{d})(c+d+e)(\bar{a}+b+c+d)$$

$$\text{Cost} = 6 + 1 + 3 \times 5 + 4 \times 1 + 6 = 32$$

POS is minimum cost

Problem 1 (Alternative solution)

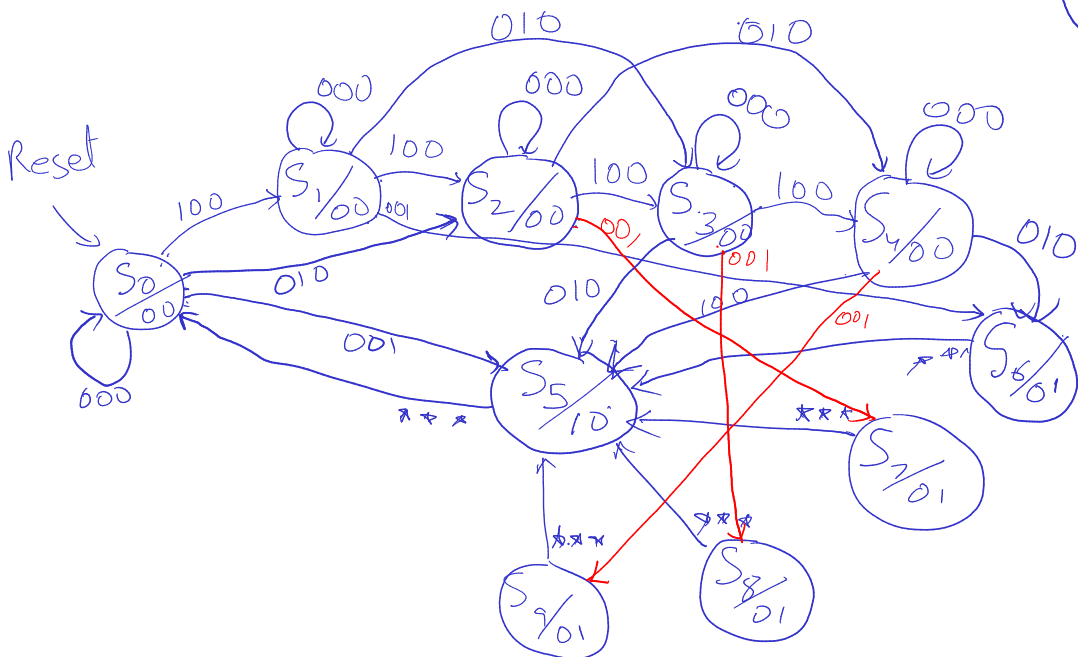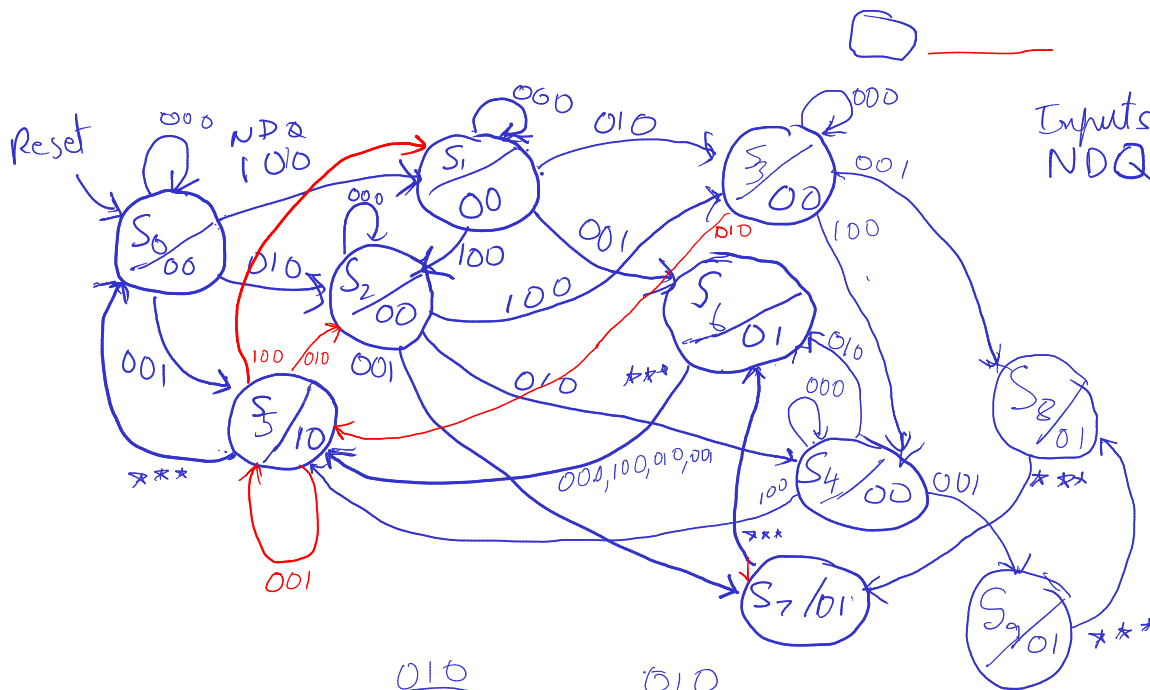

Money inserted (cents)	Change due (cents)	PS	NS Inputs (NDQ)				output (RC)
			000	100	010	001	
0	0	S ₀	S ₀	S ₁	S ₂	S ₅	00
5	0	S ₁	S ₁	S ₂	S ₃	S ₆	00
10	0	S ₂	S ₂	S ₃	S ₄	S ₇	00
15	0	S ₃	S ₃	S ₄	S ₅	S ₈	00
20	0	S ₄	S ₄	S ₅	S ₆	S ₉	00
25	0	S ₅	S ₀	S ₀	S ₀	S ₀	10
30	5	S ₆	S ₅	S ₅	S ₅	S ₅	01
35	10	S ₇	S ₆	S ₆	S ₆	S ₆	01
40	15	S ₈	S ₇	S ₇	S ₇	S ₇	01
45	20	S ₉	S ₈	S ₈	S ₈	S ₈	01