


# 8 Karnaugh maps = (truth table + Venn diagram)

## 8.1 Two input K-maps

		A	
		0	1
B	0	$m_0$	$m_2$
	1	$m_1$	$m_3$

XOR gate



$x_1$	$x_2$	$f$
0	0	0
0	1	1
1	0	1
1	1	0

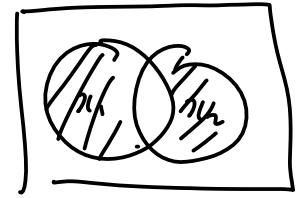

## 8.2 Three input K-maps


$0 \quad 1 \quad 3 \rightarrow 2$

		AB			
		00	01	11	10
C	0	$m_0$	$m_2$	$m_6$	$m_4$
	1	$m_1$	$m_3$	$m_7$	$m_5$

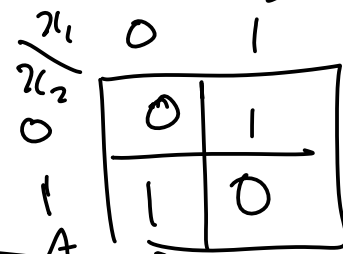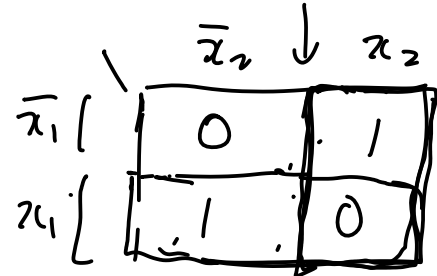

## 8.3 Four input K-maps

		AB			
		00	01	11	10
CD	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

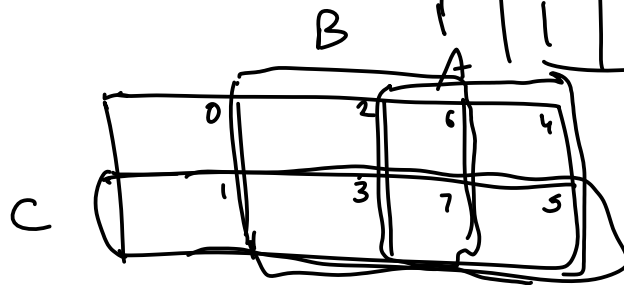

## 8.4 Five input K-maps


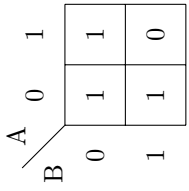

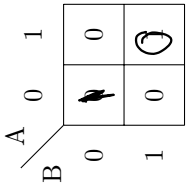

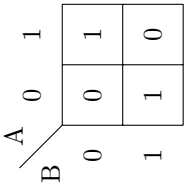
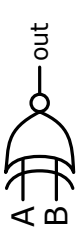
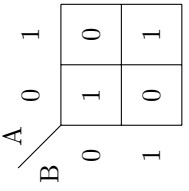
A = 0

		BC			
		00	01	11	10
DE	00	$m_0$	$m_4$	$m_{12}$	$m_8$
	01	$m_1$	$m_5$	$m_{13}$	$m_9$
	11	$m_3$	$m_7$	$m_{15}$	$m_{11}$
	10	$m_2$	$m_6$	$m_{14}$	$m_{10}$

A = 1


		BC			
		00	01	11	10
DE	00	$m_{16}$	$m_{20}$	$m_{28}$	$m_{24}$
	01	$m_{17}$	$m_{21}$	$m_{29}$	$m_{25}$
	11	$m_{19}$	$m_{23}$	$m_{31}$	$m_{27}$
	10	$m_{18}$	$m_{22}$	$m_{30}$	$m_{26}$

## 9 More Gates and notations summary

Name	C/Verilog	Boolean expr.	Truth Table	(ANSI) symbol	K-map															
NAND Gate	$Q = \sim(x1 \& x2)$	$Q = \overline{x_1 \cdot x_2} = \overline{x_1}x_2$	<table border="1"> <thead> <tr> <th><math>x_1</math></th> <th><math>x_2</math></th> <th><math>\overline{x_1 \cdot x_2}</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	$x_1$	$x_2$	$\overline{x_1 \cdot x_2}$	0	0	1	0	1	1	1	0	1	1	1	0		
$x_1$	$x_2$	$\overline{x_1 \cdot x_2}$																		
0	0	1																		
0	1	1																		
1	0	1																		
1	1	0																		
NOR Gate	$Q = \sim(x1   x2)$	$Q = \overline{x_1 + x_2}$	<table border="1"> <thead> <tr> <th><math>x_1</math></th> <th><math>x_2</math></th> <th><math>\overline{x_1 + x_2}</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	$x_1$	$x_2$	$\overline{x_1 + x_2}$	0	0	1	0	1	0	1	0	0	1	1	0		
$x_1$	$x_2$	$\overline{x_1 + x_2}$																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	0																		
XOR Gate	$Q = x1 \wedge x2$	$Q = x_1 \oplus x_2$	<table border="1"> <thead> <tr> <th><math>x_1</math></th> <th><math>x_2</math></th> <th><math>x_1 \oplus x_2</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>0</td> </tr> <tr> <td>0</td> <td>1</td> <td>1</td> </tr> <tr> <td>1</td> <td>0</td> <td>1</td> </tr> <tr> <td>1</td> <td>1</td> <td>0</td> </tr> </tbody> </table>	$x_1$	$x_2$	$x_1 \oplus x_2$	0	0	0	0	1	1	1	0	1	1	1	0		
$x_1$	$x_2$	$x_1 \oplus x_2$																		
0	0	0																		
0	1	1																		
1	0	1																		
1	1	0																		
XNOR Gate	$Q = \sim(x1 \wedge x2)$	$Q = \overline{x_1 \oplus x_2}$	<table border="1"> <thead> <tr> <th><math>x_1</math></th> <th><math>x_2</math></th> <th><math>\overline{x_1 \oplus x_2}</math></th> </tr> </thead> <tbody> <tr> <td>0</td> <td>0</td> <td>1</td> </tr> <tr> <td>0</td> <td>1</td> <td>0</td> </tr> <tr> <td>1</td> <td>0</td> <td>0</td> </tr> <tr> <td>1</td> <td>1</td> <td>1</td> </tr> </tbody> </table>	$x_1$	$x_2$	$\overline{x_1 \oplus x_2}$	0	0	1	0	1	0	1	0	0	1	1	1		
$x_1$	$x_2$	$\overline{x_1 \oplus x_2}$																		
0	0	1																		
0	1	0																		
1	0	0																		
1	1	1																		

NAND gate

A	B	f
0	0	1
0	1	1
1	0	1
1	1	0

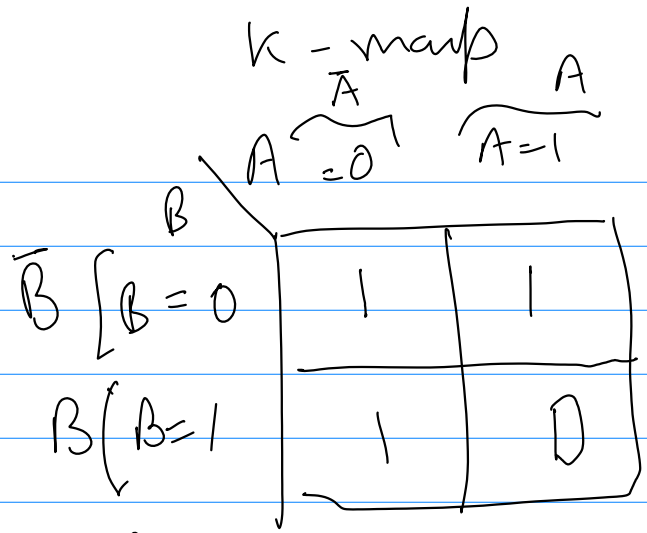


NOR gate  
OR  $\rightarrow$  NOT

$$f = A + B$$

K-map

A	B	g	f
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

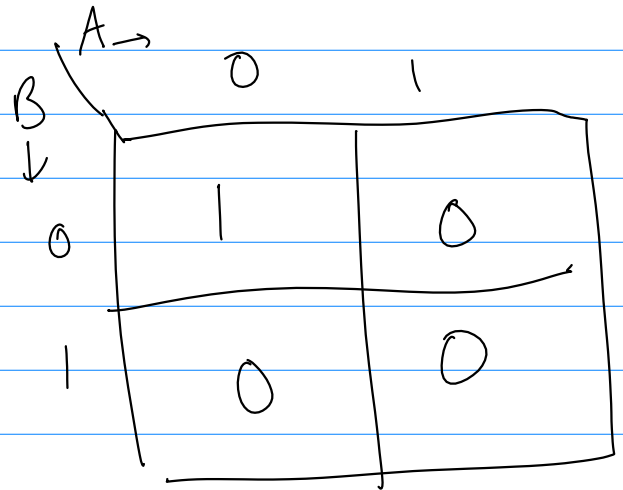


$\overrightarrow{A, B, C, D}$

Example 10. Convert the following Boolean expression into a K-map.  $f = \overline{AB + CD}$

$f = m_1 + m_5 + m_{13}$

$f =$

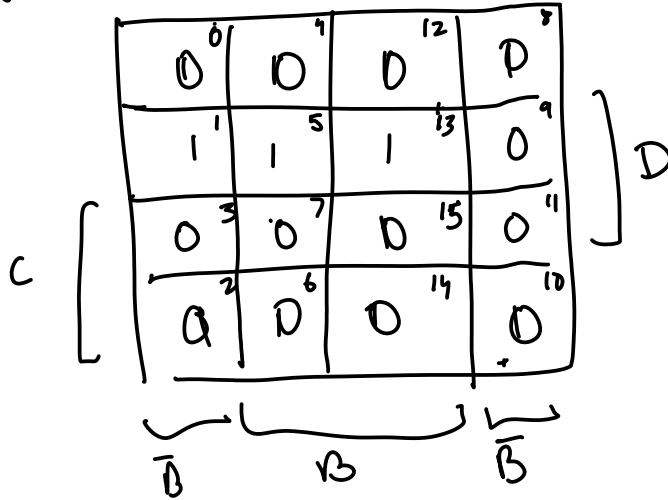


$g_1 = A\bar{B}$

$g_2 = g_1 + C$

$g_3 = \overline{g_2}$

$f = g_3 \cdot D$

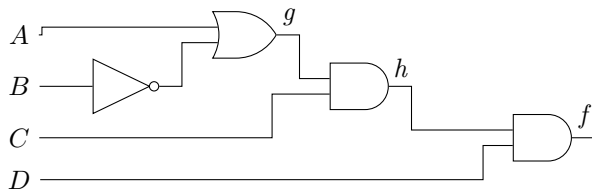
Problem 10. Convert the following logic circuit into a K-map.



## 10 Boolean Algebra

### 10.1 Axioms of Boolean algebra

1.  $0 \cdot 0 = 0$
2.  $1 + 1 = 1$

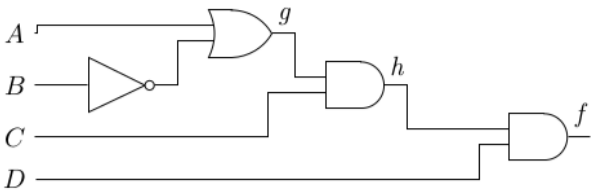


Truth table for function  $g = A + \bar{B}$ :

CD \ AB	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	1	0	1	1
10	1	0	1	1

Truth table for function  $g = A + \bar{B}$  with highlighted regions:



CD \ AB	00	01	11	10
00	1	0	1	1
01	1	0	1	1
11	1	0	1	1
10	1	0	1	1


$h = g \cdot C$

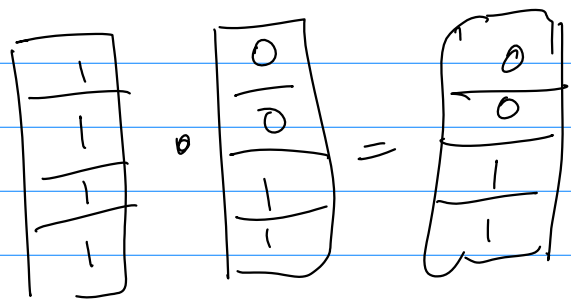

Truth table for function  $A = \bar{C}$ :

CD \ AB	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	0	0	0	0
10	0	0	0	0

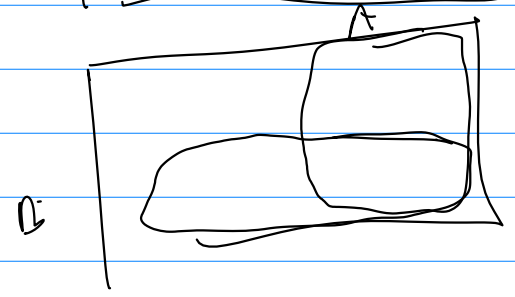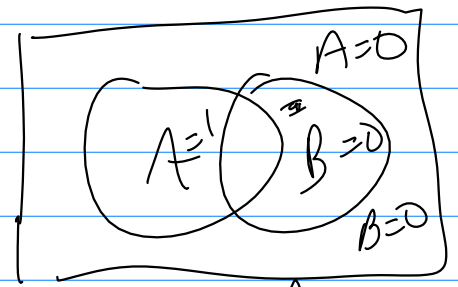


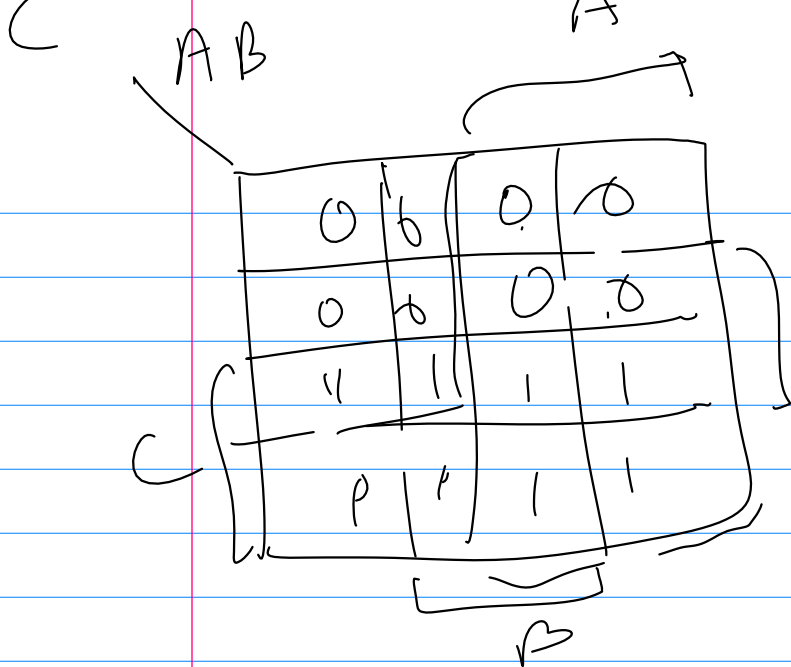

$f =$

$$f = h \cdot D$$

$$= (A + \bar{B}) C \cdot D$$

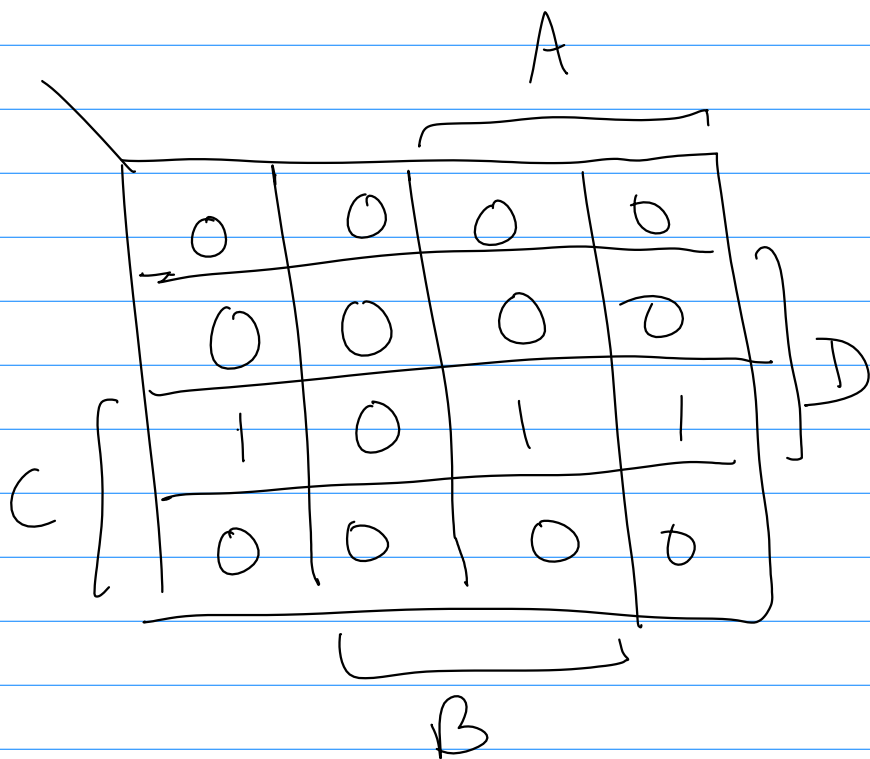

3.  $1 \cdot 1 = 1$

4.  $0 + 0 = 0$

5.  $0 \cdot 1 = 1 \cdot 0 = 0$

6.  $\bar{0} = 1$

7.  $\bar{1} = 0$

8.  $x = 0$  if  $x \neq 1$

9.  $x = 1$  if  $x \neq 0$

## 10.2 Single variable theorems (Prove by drawing K-maps)

1.  $x \cdot 0 = 0$

2.  $x + 1 = 1$

3.  $x \cdot 1 = x$

4.  $x + 0 = x$

5.  $x \cdot x = x$

6.  $x + x = x$

7.  $x \cdot \bar{x} = 0$

8.  $x + \bar{x} = 1$

9.  $\overline{\bar{x}} = x$

**Remark 2** (Duality). *Swap  $+$  with  $\cdot$  and  $0$  with  $1$  to get another theorem*

### 10.3 Two and three variable properties (Prove by K-maps)

1. Commutative:  $x \cdot y = y \cdot x$ ,  $x + y = y + x$

2. Associative:  $x \cdot (y \cdot z) = (x \cdot y) \cdot z$ ,  $x + (y + z) = (x + y) + z$

3. Distributive:  $x \cdot (y + z) = x \cdot y + x \cdot z$ ,  $x + y \cdot z = (x + y) \cdot (y + z)$

4. Absorption:  $x + x \cdot y = x$ ,  $x \cdot (x + y) = x$



5. Combining:  $x \cdot y + x \cdot \bar{y}, (x + y) \cdot (x + \bar{y}) = x$

6. DeMorgan's theorem:  $\overline{x \cdot y} = \bar{x} + \bar{y}, \overline{x + y} = \bar{x} \cdot \bar{y}.$

7. Concensus:


(a)  $x + \bar{x} \cdot y = x + y$

(b)  $x \cdot (\bar{x} + y) = x \cdot y$

(c)  $x \cdot y + y \cdot z + \bar{x} \cdot z = x \cdot y + \bar{x} \cdot z$

(d)  $(x + y) \cdot (y + z) \cdot (\bar{x} + z) = (x + y) \cdot (\bar{x} + z)$

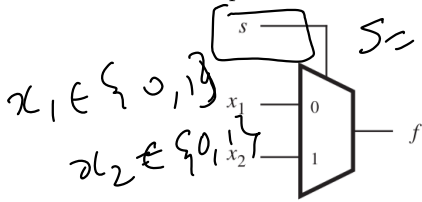**Example 11 (Multiplexer).** Multiplexer is a circuit used to select one of the input lines  $x_1$  and  $x_2$  based only select input  $s$ . When  $s = 0$ ,  $x_1$  is selected,  $x_2$  is selected otherwise. Find a boolean expression and a circuit for multiplexer



$s$	$f(s, x_1, x_2)$
0	$x_1$
1	$x_2$

$s$	$x_1$	$x_2$	$f$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

**Example 12.** Simplify  $f = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$  using boolean algebra

**Example 13.** Simplify  $f = \bar{A}\bar{A}\bar{C} + \bar{A}\bar{B}C$  using K-maps.

$S, x_1, x_2$

	$S$	$x_1$	$x_2$	$f$
0	0	0	0	0
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	0
6	1	1	0	0
7	1	1	1	1

$S, x_1, x_2$

$x_2$	$S$	$x_1$	$x_2$	$f$
0	0	1	0	0
1	0	1	3	7

$S, x_1, x_2$

$x_2$	$S$	$x_1$	$x_2$	$f$
0	0	1	0	0
1	0	1	3	7

$S, x_1, x_2$

$S$	$x_1$	$x_2$	$f$
0	1	0	0
1	1	3	7

$x_1$	$x_2$	$S$	$f$
0	1	0	0
1	1	3	7

$f$

$S, x_1, x_2$

$x_2$	$\bar{S}$	$\bar{S}$	$S$	$f$
0	0	1	0	0
1	0	1	3	7

$f = m_2 + m_3 + m_5 + m_7$

$f = x_1 \cdot \bar{S}$   
 $+ x_2 x_1 \leftarrow \text{unnecessary}$   
 $+ x_2 \cdot S$

$f = x_1 \cdot \bar{S} + x_2 S$