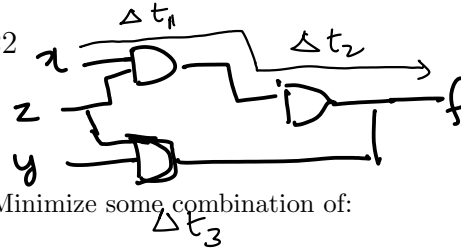


Logic minimization: Minimum-cost circuits

Vikas Dhiman for ECE275


September 19, 2022



1 Logic minimization

A general optimization criteria for multi-level logic are to Minimize some combination of:


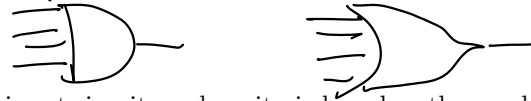
1. Area occupied by the logic gates and interconnect;
2. the Critical Path Delay of the longest path through the logic;
3. the Degree of Testability of the circuit, measured in terms of the percentage of faults covered by a specified set of test vectors, for an appropriate fault model (Eg., single stuck faults, multiple stuck faults, etc.);
4. Power consumed by the logic gates.



In this course, we will start with two-level multi-input circuits and a criteria based on the number of gates/transistors/diodes.

2 Programmable Logic Arrays (PLA)

Two level circuit

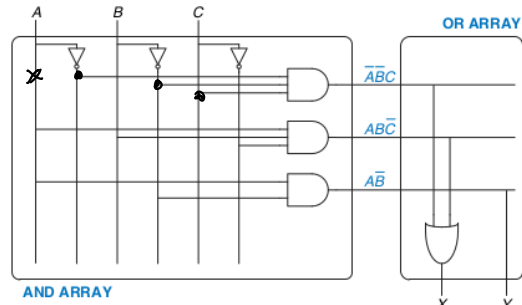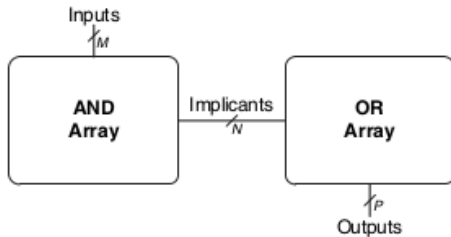

sum of products form

3 Two-level circuits

The cost that we are going to consider in this class depend upon:


1. Number of gates.
2. Number of input to the gates.

More gates need more transistors, more area on the chip. More-inputs the gate need more transistors within each gate. Number of gate inputs can be considered secondary criterion to the number of gates.

Example 1. Find the cost of the following Boolean expression $X = \overline{A}BC + A\overline{B}C + A\overline{B}$.

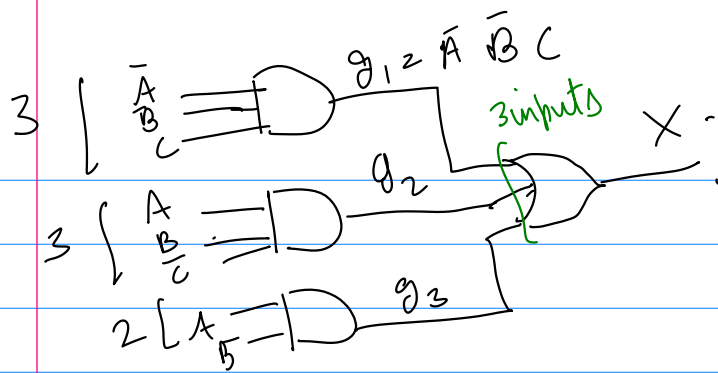Problem 1. Find the cost of the following Boolean expression $X = A\overline{B}C + \overline{A}B\overline{C} + \overline{B}C$.

*1 and + 1 and + 1 and = 3 and gates } 4 gates
= 1 OR gate }*



$$X = g_1 + g_2 + g_3$$

4 gates


Total Number of inputs

$$= \underbrace{3+3+2}_{\text{AND}} + \underbrace{3}_{\text{OR}}$$

$$\begin{aligned} &= 8+3 = 11 \\ \text{Total cost} &= 4+11 = 15 \end{aligned}$$

OR = Union of regions

$$f = m_0 + m_1 + m_2 + m_3 + m_7$$

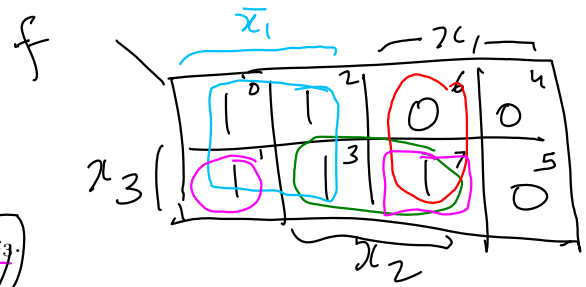

4 Terminology for K-maps

Running Example: $f = \sum m(0, 1, 2, 3, 7)$

Literal A single variable or its complement. Example: \bar{x}_1, x_1, x_2, x_3

Implicant A product term which is true for a function. All minterms are implicants. Example:

$$x_1x_2x_3, \bar{x}_1, m_0 = \bar{x}_1\bar{x}_2\bar{x}_3, \bar{x}_1x_3, \bar{x}_1\bar{x}_3.$$

x_1, x_2 ✗

x_2x_3 ✓

\bar{x}_1 ✓

Prime Implicant An implicant that cannot be combined into fewer literals. Example: $\bar{x}_1, x_2x_3.$

Essential Prime Implicant An implicant that cannot be combined into fewer literals. Example:

$$x_2x_3.$$

$m_1 = \bar{x}_1\bar{x}_2x_3$ ✓

Cover : List of Prime Implicants that account for all $f = 1$.

Cost : Number of gates (excluding not gate on literals) and number of inputs to each gate.

Example 2. Find minimum cost expression for the function $f(x_1, x_2, x_3) = \prod M(4, 5, 6)$

Mm, cost expression from K-map

① Find all PI

② Find all EPI

③ $f = \sum EPI +$

④ Do EPIs cover all $f=1$

y (4) is false



Petricks methods

Problem 2. Find minimum cost expression for the function $f(x_1, x_2, x_3) = \prod M(2, 5, 6)$

4.1 Incompletely specified functions or Don't cares



Figure 1: 7 Segment Representations of Each Integer

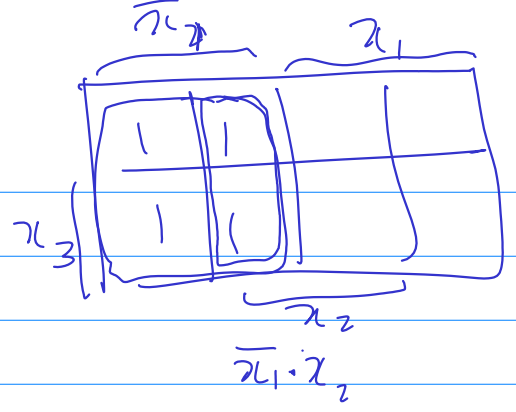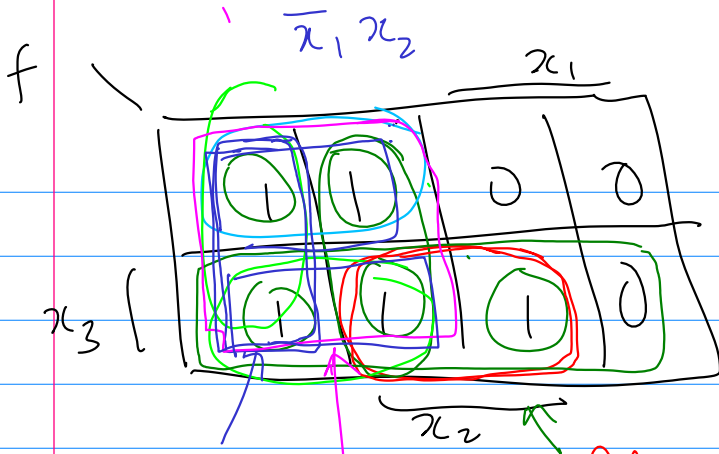


NOT PI
 $= \bar{x}_1 \bar{x}_2$

PRIME IMPLICANT (fewest literals)
 $= x_2 x_3$

PI = \bar{x}_1


= fewest inputs
 = lowest cost

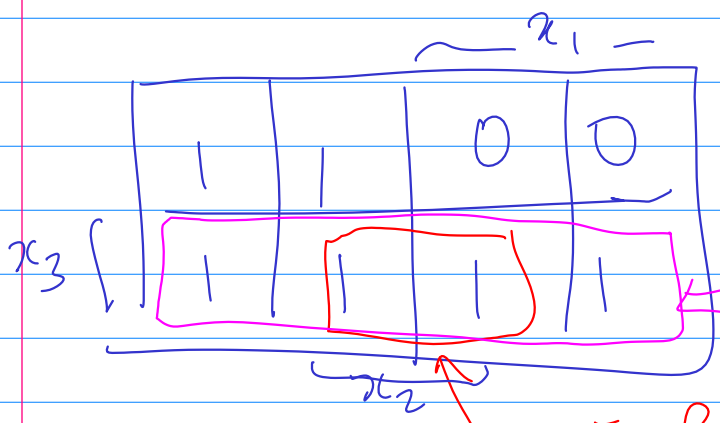

PI = x_3


NOT PI
 $x_2 x_3$

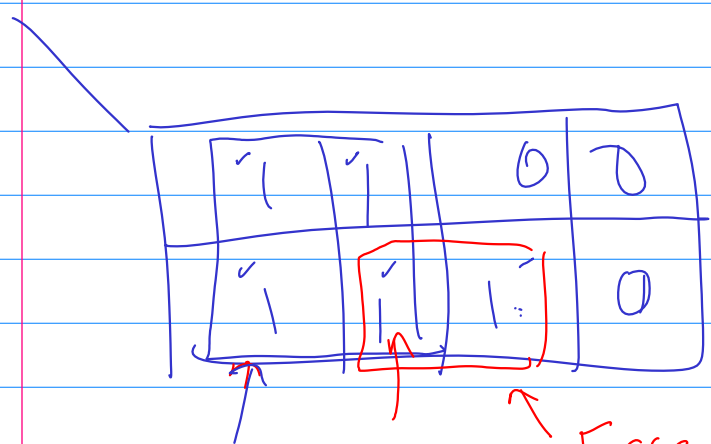lower powers of 2 = 2, 4, 8, 16, 32
 EPI
 PI₃



Essential PI
 EPI

Essential PI
 EPI

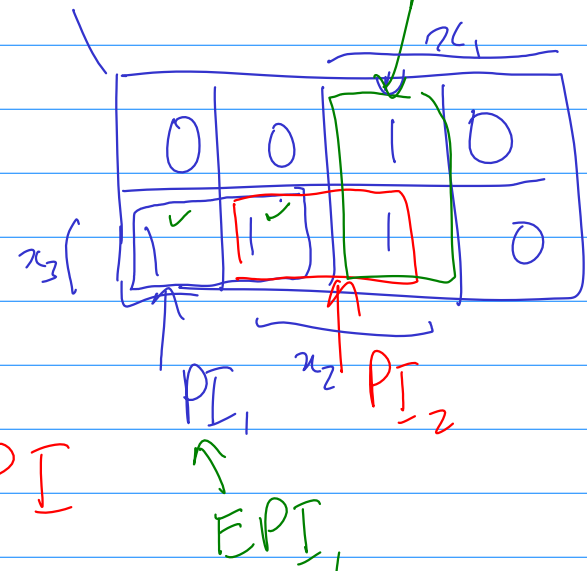


PI₁
 EPI₁
 PI₂

$$f(x_1, x_2, x_3) = \prod M(4, 5, 6)$$

Maxterms

x_1	x_2	x_3	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

f

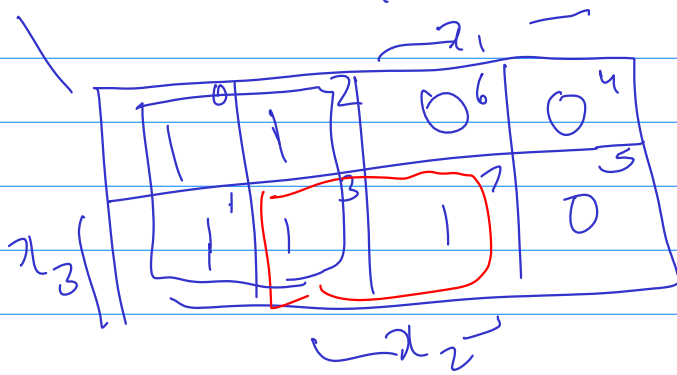

① PIs
 x_2, x_2x_3

② FPIs
 \bar{x}_1, x_2x_3

③ $f = \bar{x}_1 + x_2x_3$
 (4) Stop
 #2
 OR gate

Cost of $f = 2 \text{ gates} + 4 \text{ inputs}$

$$= 6$$

BCD Value				LED Segment
D_3	D_2	D_1	D_0	E
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	d
1	0	1	1	d
1	1	0	0	d
1	1	0	1	d
1	1	1	0	d
1	1	1	1	d

Example 3. Find minimum cost expression for the function

$$f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

Problem 3. Find minimum cost expression for the function

$$f(x_1, \dots, x_4) = \sum m(0, 2, 4, 6, 7, 8, 9, 13) + D(1, 12, 15)$$