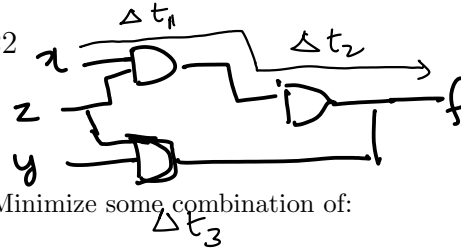


Logic minimization: Minimum-cost circuits

Vikas Dhiman for ECE275


September 19, 2022



1 Logic minimization

A general optimization criteria for multi-level logic are to Minimize some combination of:


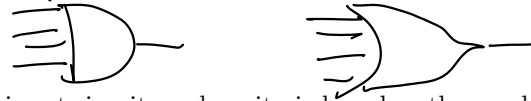
1. Area occupied by the logic gates and interconnect;
2. the Critical Path Delay of the longest path through the logic;
3. the Degree of Testability of the circuit, measured in terms of the percentage of faults covered by a specified set of test vectors, for an appropriate fault model (Eg., single stuck faults, multiple stuck faults, etc.);
4. Power consumed by the logic gates.



In this course, we will start with two-level multi-input circuits and a criteria based on the number of gates/transistors/diodes.

2 Programmable Logic Arrays (PLA)

Two level circuit

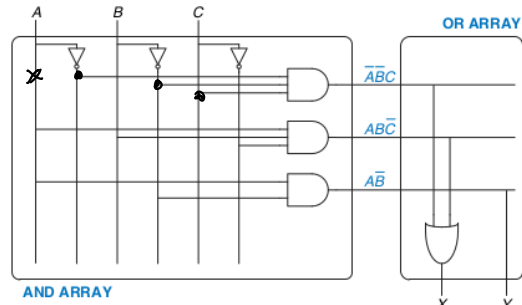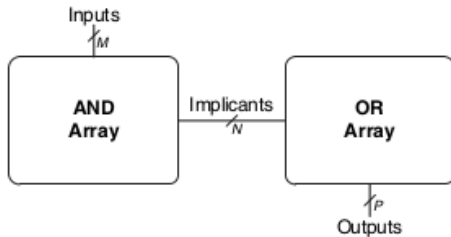

sum of products form

3 Two-level circuits

The cost that we are going to consider in this class depend upon:


1. Number of gates.
2. Number of input to the gates.

More gates need more transistors, more area on the chip. More-inputs the gate need more transistors within each gate. Number of gate inputs can be considered secondary criterion to the number of gates.

Example 1. Find the cost of the following Boolean expression $X = \overline{A}BC + A\overline{B}C + A\overline{B}$.

*1 and + 1 and + 1 and = 3 and gates } 4 gates
= 1 OR gate*

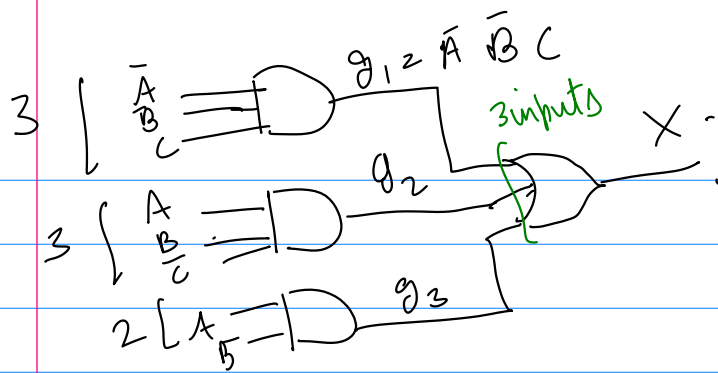Problem 1. Find the cost of the following Boolean expression $X = A\overline{B}C + \overline{A}B\overline{C} + \overline{B}C$.



$$X = g_1 + g_2 + g_3$$

4 gates

Total Number of inputs


$$= \underbrace{3+3+2}_{\text{AND}} + \underbrace{3}_{\text{OR}}$$

$$= 8+3 = 11$$

$$\text{Total cost} = 4+11 = 15$$

OR = Union of regions

$$f = m_0 + m_1 + m_2 + m_3 + m_7$$

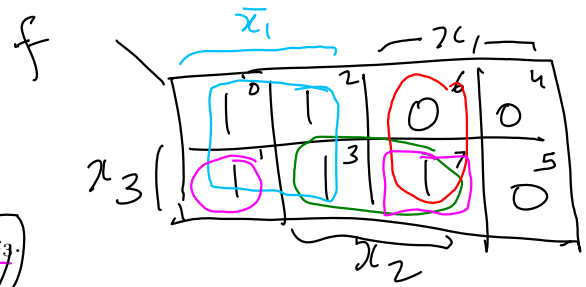

4 Terminology for K-maps

Running Example: $f = \sum m(0, 1, 2, 3, 7) = \bar{x}_1 + x_1 x_2 x_3$

Literal A single variable or its complement. Example: \bar{x}_1, x_1, x_2, x_3

Implicant A product term which is true for a function. All minterms are implicants. Example:

$$x_1 x_2 x_3, \bar{x}_1, m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3, \bar{x}_1 x_3, \bar{x}_1 \bar{x}_3.$$

x_1, x_2 ✗

$x_2 x_3$ ✓

\bar{x}_1 ✓

Prime Implicant An implicant that cannot be combined into fewer literals. Example: $\bar{x}_1, x_2 x_3$.

Essential Prime Implicant An implicant that cannot be combined into fewer literals. Example:

$$x_2 x_3.$$


$m_1 = \bar{x}_1 \bar{x}_2 x_3$ ✓

Cover : List of Prime Implicants that account for all $f = 1$.

Cost : Number of gates (excluding not gate on literals) and number of inputs to each gate.

Example 2. Find minimum cost expression for the function $f(x_1, x_2, x_3) = \prod M(4, 5, 6)$

① Fnd SOP

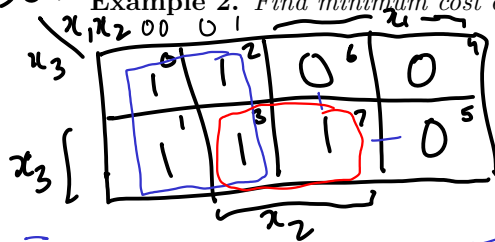

PIs: $\bar{x}_1, x_2 x_3$

EPIs: $\bar{x}_1, x_2 x_3$

$$f = \bar{x}_1 + x_2 x_3$$

Problem 2. Find minimum cost expression for the function $f(x_1, x_2, x_3) = \prod M(2, 5, 6)$

① Fnd SOP

② Fnd POS

Making a K-map

Finding EPIs + PIs → shortest

① Find min SOP

② " min POS

③ Choose best among

then



x_1	x_2	x_3	f
0	0	0	0
0	0	1	1
0	1	0	0

$f = \prod M(0, 2, \dots)$

4.1 Incompletely specified functions or Don't cares



Figure 1: 7 Segment Representations of Each Integer

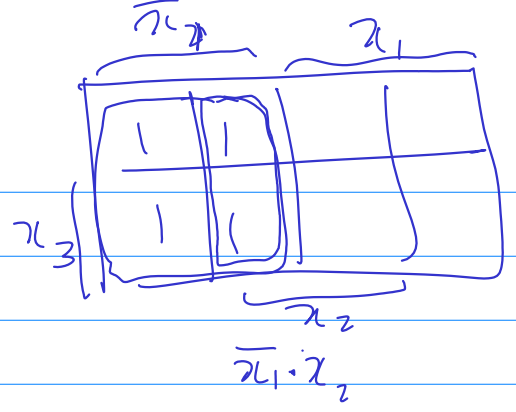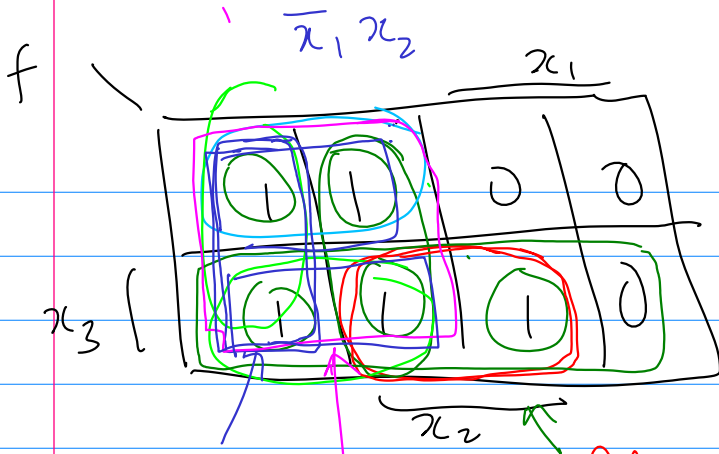


NOT PI
= $\bar{x}_1 \bar{x}_2$

PRIME IMPLICANT (fewest literals)
= $x_2 x_3$

PI = \bar{x}_1

= fewest inputs
= lowest cost

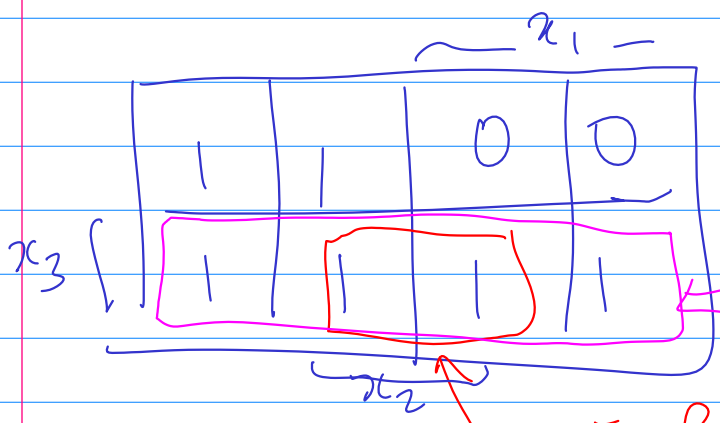


PI = x_3

NOT PI
 $x_2 x_3$


powers of 2 = 2, 4, 8, 16, 32

EPI
PI₃

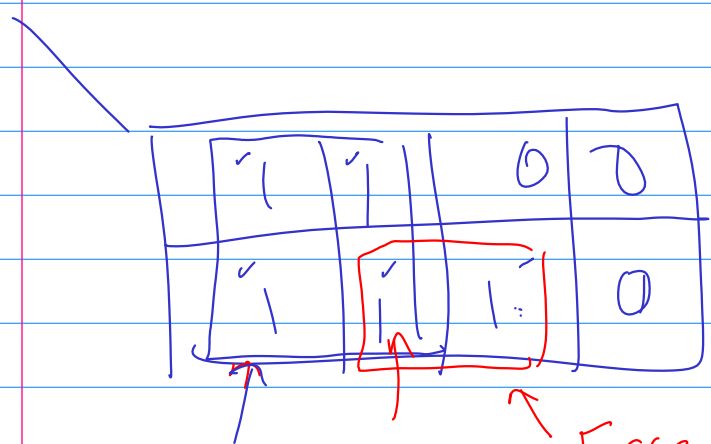

Essential PI
EPI

Essential PI
EPI

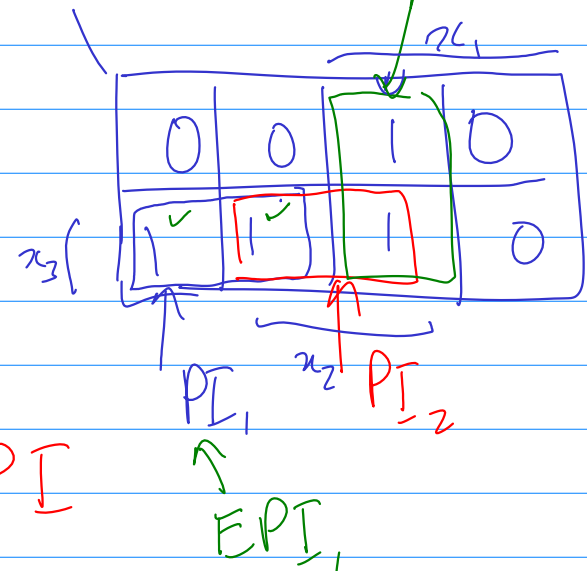


PI₁
EPI₁
PI₂

$$f(x_1, x_2, x_3) = \prod M(4, 5, 6)$$

Maxterms

x_1	x_2	x_3	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

f

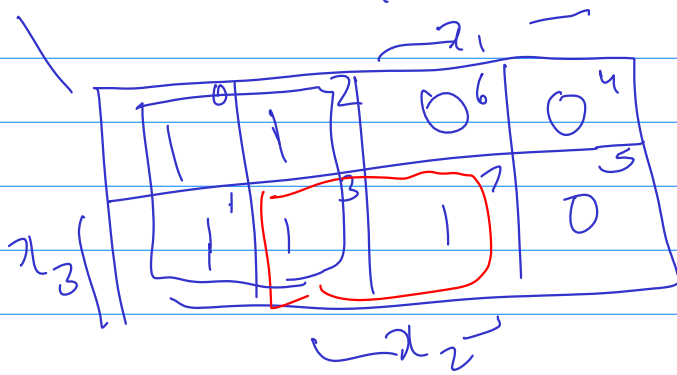

① PIs


$$x_1, x_2, x_3$$

② FPIs

$$\bar{x}_1, x_2, x_3$$

③ $f = \bar{x}_1 + x_2 x_3$

④ Stop

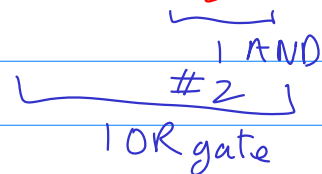

Cost of $f = 2 \text{ gates} + 4 \text{ inputs} \# 2$

$$= 6$$

BCD Value				LED Segment
D_3	D_2	D_1	D_0	E
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	d
1	0	1	1	d
1	1	0	0	d
1	1	0	1	d
1	1	1	0	d
1	1	1	1	d

Example 3. Find minimum cost expression for the function


$$f(x_1, \dots, x_4) = \sum m(2, 4, 5, 6, 10) + D(12, 13, 14, 15)$$

Problem 3. Find minimum cost expression for the function

$$f(x_1, \dots, x_4) = \sum m(0, 2, 4, 6, 7, 8, 9, 13) + D(1, 12, 15)$$

SOP form

Min. cost expression from K-map

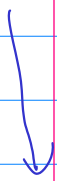

① Find all PI

② Find all EPI

③ $f = \sum \overline{EPI}$ +

④ Do EPIs cover all $f=1$

if ④ is false

Patrick's methods

1. Find SOP

	x_1, x_2	00	01	x_2	
x_3		0	1	2	3
		1	1	0	0
x_3		1	1	1	0
		1	1	1	0
		1	1	1	0

PIs: $\bar{x}_1, x_2 x_3$; EPIs: $\bar{x}_1, x_2 x_3$
 $f = \bar{x}_1 + x_2 x_3$

- ① Find min SOP
- ② " min POS
- ③ Choose best among them $\frac{x_1 x_2 x_3}{0 0 0} \frac{f}{0}$

2. Find POS

Demorgan theorem

① Obs: POS is a Demorgan complement of SOP

$f = \bar{x}_1 + x_2 x_3$ ← SOP

Take complement on both sides

$\bar{f} = \overline{\bar{x}_1 + x_2 x_3} = \bar{x}_1 \cdot \overline{x_2 x_3} = \bar{x}_1 \cdot (\bar{x}_2 + \bar{x}_3)$ ← POS

f

	x_1, x_2	00	01	x_2	
x_3		0	1	2	3
		1	1	0	0
x_3		1	1	1	0
		1	1	1	0
		1	1	1	0

\bar{f}

	x_1, x_2	00	01	x_2	
x_3		0	0	1	1
		0	0	0	0
x_3		0	0	1	1
		0	0	1	1
		0	0	1	1

$\bar{f} = \text{SOP} =$
 ↓ Demorgan theorem

$f = \text{POS}$

PIs = $x_1 \bar{x}_3, x_1 \bar{x}_2$

EPIs = $x_1 \bar{x}_3, x_1 \bar{x}_2$

$\bar{f} = x_1 \bar{x}_3 + x_1 \bar{x}_2$

$\bar{f} = \overline{x_1 \bar{x}_3 + x_1 \bar{x}_2}$

$f = (\bar{x}_1 + x_3) \cdot (\bar{x}_1 + x_2)$ ← POS

Confusions

Maxterm

f

	x_1, x_2	00	01	x_2	
x_3		0	1	2	3
		0	1	0	0
x_3		1	1	1	0
		1	1	1	0
		1	1	1	0

Annotations:
 - Blue circle around (0,2) and (0,3) labeled $(\bar{x}_1 + x_3)$
 - Red circle around (1,2) and (1,3) labeled $(x_2 + \bar{x}_1)$

$f = (\bar{x}_1 + x_3) (x_2 + \bar{x}_1)$

Following rules for labeling maxterms

$$f = \bar{x}_1 + \underbrace{x_2 x_3}_{1+2m} \leftarrow \text{SOP}$$

$$f = \underbrace{(\bar{x}_1 + x_3)}_{1g+2m} \cdot \underbrace{(x_1 + x_2)}_{1g+2m} \leftarrow \text{POS}$$

Cost of SOP form = $3 + 3 \stackrel{1g+2m}{=} 6$

Cost of POS form = $3 + 3 + 3 = 9$

Min cost expression is SOP form $f = \bar{x}_1 + x_2 x_3$

f

	x_1	0	1	0	1
x_3	0	1	1	1	0

Annotations: x_1 (top), x_2 (bottom), x_3 (left). Prime marks are present on the 1s in the top row and the 1s in the bottom row.

$$f = \text{ITM}(2, 5, 6)$$

PIs: $\bar{x}_1 \bar{x}_2, \bar{x}_1 x_3, x_2 x_3, \bar{x}_2 \bar{x}_3$

EPIs: $x_2 x_3, \bar{x}_2 \bar{x}_3$

$$f = x_2 x_3 + \bar{x}_2 \bar{x}_3 + \bar{x}_1 \bar{x}_2 \quad \leftarrow \text{min SOP}$$

min POS

\bar{f}

	x_1	0	1	0
x_3	0	0	0	1

Annotations: x_1 (top), x_2 (bottom), x_3 (left). Prime marks are present on the 1s in the top row and the 1 in the bottom row.

EPIs = PIs = $x_2 \bar{x}_3, \bar{x}_1 \bar{x}_2 x_3$

$$\bar{f} = x_2 \bar{x}_3 + \bar{x}_1 \bar{x}_2 x_3$$

↓ DeMorgan's complement

$$f = (\bar{x}_2 + x_3) \cdot (\bar{x}_1 + x_2 + \bar{x}_3)$$

min POS

Cost of SOP form:

$$\underbrace{x_2 x_3}_{1g+2in} + \underbrace{\bar{x}_2 \bar{x}_3}_{1g+2in} + \underbrace{\bar{x}_1 \bar{x}_2}_{1g+2in}$$

$$\underbrace{\hspace{10em}}_{1g+3in}$$

$$= 3 + 3 + 3 + 4 = 13$$

$$\text{Cost of POS form n: } f = \underbrace{(\bar{x}_2 + x_3)}_{|g+2\text{in}}} \cdot \underbrace{(\bar{x}_1 + x_2 + \bar{x}_3)}_{|g+3\text{in}} \\ \underbrace{\hspace{10em}}_{|g+2\text{in}}$$

Min cost extra is POS form = 3 + 4 + 3 = 10

$$f = (\bar{x}_2 + x_3) \cdot (\bar{x}_1 + x_2 + \bar{x}_3)$$