

Analog details behind the digital abstraction

Vikas Dhiman for ECE275


October 17, 2022

Some of the material is out of the textbook. Additional resources include Appendix B of Brown and Vranesic book, "Fundamentals of digital logic."

1 Objectives

1. Describe how tri-state and open-collector outputs are different from totem-pole outputs
2. Compute noise margin of one device driving the same time
3. Understand timing diagrams, gate delays and critical path
4. Design Hazard-free two level circuits

2 Logic levels and Noise Margins

 

Definition 1 (Supply Voltage ($V_{DD}/V_{CC}/V_{SS}$)).

Highest voltage in the DC circuit

Definition 2 (Ground Voltage (V_{GND})).

= 0

Definition 3 (Input high (V_{IH}) and Input Low (V_{IL}) of a gate).

V_{IH} is the voltage above which the gate considers the logic level to be "HIGH"

$$0 - 5V$$

minimum

$$V_{IH} = 2.5V$$

$$V_{IL} = 2.5V$$


$$V_{OH} = 5V$$

$$V_{OL} = 0V$$

Definition 4 (Output high (V_{OH}) and Output low (V_{OL}) of gate).

V_{OH} is the voltage that the gate will output for a "high" output

 Definition 5 (Positive logic and Negative logic).



Definition 6 (Noise margins (NM_L and NM_H) of a channel).

$$NM_H = |V_{OH} - V_{IH}| \geq 0$$

$$NM_L = |V_{IL} - V_{OL}| \geq 0$$

fan-out capacity

Example 1.

If $V_{DD} = 5V$, $V_{IL} = 1.35V$, $V_{IH} = 3.15V$, $V_{OL} = 0.33V$ and $V_{OH} = 3.84V$ for both the "inverters", then what are the low and high noise margins? Can the circuit tolerate 1V of noise at the channel?

$$NM_H = V_{OH} - V_{IH} = 3.84 - 3.15 = 0.69V$$

$$NM_L = V_{IL} - V_{OL} = 1.35 - 0.33 = 1.02V$$


3 Semiconductors and Doping

Not in syllabus but good to know


Elements recognized as metalloids					V.T.E
13	14	15	16	17	
Boron	Carbon	Nitrogen	Oxygen	Fluorine	
Aluminum	Silicon	Phosphorus	Sulfur	Chlorine	Non metal
Gallium	Germanium	Arsenic	Selenium	Bromine	
In	Tin	Antimony	Tellurium	Iodine	
Thallium	Pb	Bismuth	Polonium	Astatine	

Commonly recognized (86-99%): B, Si, Ge, As, Sb, Te
 Irregularly recognized (40-49%): Po, At
 Less commonly recognized (24%): Se
 Rarely recognized (8-10%): C, Al
 (All other elements cited in less than 6% of sources)
 Arbitrary metal-nonmetal dividing line: between Be and B, Al and Si, Ge and As, Sb and Te, Po and At


o Si o 1 2 3
 o 2, 8, 4
 6.

 

 
4 MOSFET: Metal Oxide Field Effect Transistors




5 DC Transfer characteristic

 



(a) NMOS NOT gate


 


(b) $V_x = 5 \text{ V}$

 


$$V_{I_L} = V_{I_H} = 2.5$$

  


  

Example 2. Draw a NOT gate using nMOS transistors.

 

Example 3. Draw a NOT gate using pMOS transistors.

 

Remark 1. nMOS transistors pass 0's well (output between 0 and $V_{DD} - V_t$). pMOS transistors pass 1's well (output between V_t and V_{DD}).

Example 4. Draw CMOS NOT Gate.

Example 5. Draw a two input CMOS NAND Gate


Definition 7 (Negative logic).

Example 6. Analyze the above circuit under negative logic.


Example 7. Draw a three input NAND using CMOS.

Example 8. Draw a three input NOR using CMOS.

 Example 9. Draw a two input AND gate using CMOS.



5.1 Gates with floating output

 

Definition 8 (Transmission gate). Draw a schematic of transmission gate and truth table for transmission gate. What is its commonly used symbol?

Definition 9 (Tristate buffer). *What is tristate buffer? Draw it's symbol and truth table? Where is it used?*

Example 10. *Draw a Multiplexer using transmission gates.*

Example 11. *Draw a Multiplexer using tristate buffers.*

Definition 10 (Totem-pole). *Draw a Push-pull (or Totem-pole) output NAND gate using CMOS. Can you connect this gate to a shared bus?*

Definition 11 (Tristate). *Draw a Tristate output NAND gate using CMOS with an output enable (OE) input. Can you connect this gate to a shared bus?*

Definition 12 (Open-collector). *Draw a open-collector output NAND gate. Can you connect this gate to a shared bus?*

6 Verilog truth tables

Table 11-11—Bitwise binary AND operator

&	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x


Table 11-12—Bitwise binary OR operator

	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

7 Timing diagrams and propagation delays

Example 12 (Timing diagram). *Draw a timing diagram for an ideal NAND gate.*


7.1 Delays

 

Definition 13 (Propagation delay (t_{pd})).


Definition 14 (Contamination delay (t_{cd})).

7.2 Paths

 

Example 13. Find the propagation delay of the circuit above given that propagation delay of each gate is 100ps add contamination delay of 60ps.

8 Glitches or Hazards

 

Definition 15 (Glitch or Hazard).

Example 14. Design a circuit that fixes the glitch in the above circuit (also known as glitch-free or hazard-free circuit).