

Analog details behind the digital abstraction

Vikas Dhiman for ECE275


October 17, 2022

Some of the material is out of the textbook. Additional resources include Appendix B of Brown and Vranesic book, "Fundamentals of digital logic."

1 Objectives

1. Describe how tri-state and open-collector outputs are different from totem-pole outputs
2. Compute noise margin of one device driving the same time
3. Understand timing diagrams, gate delays and critical path
4. Design Hazard-free two level circuits

2 Logic levels and Noise Margins

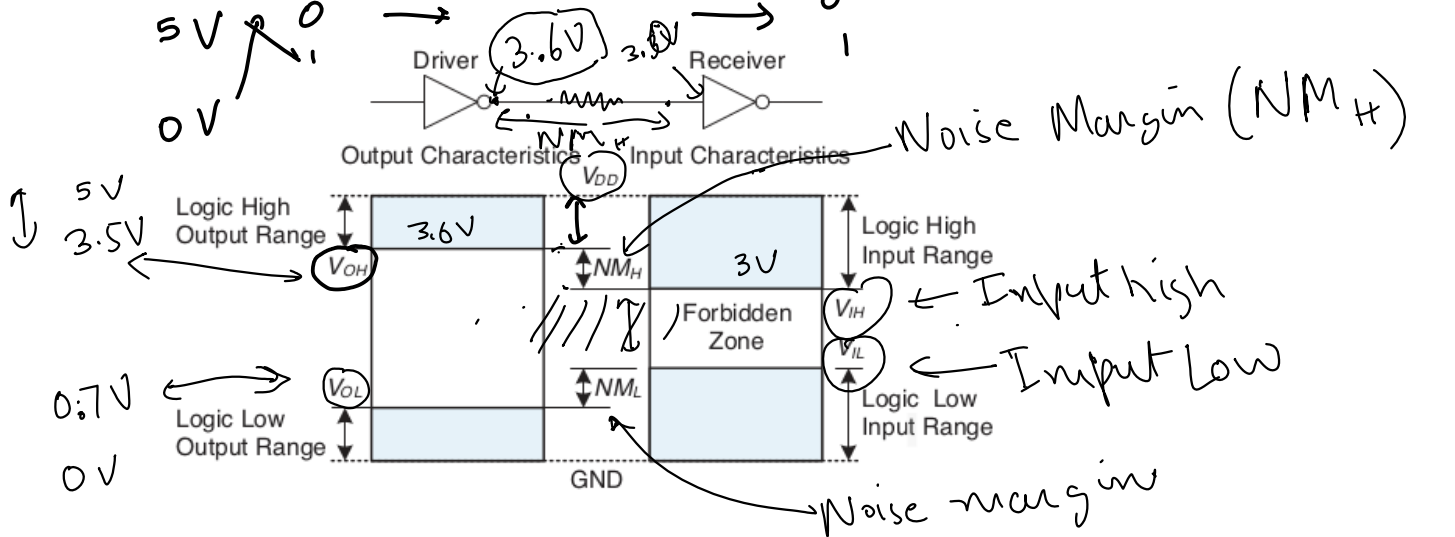

Definition 1 (Supply Voltage ($V_{DD}/V_{CC}/V_{SS}$)).

Highest voltage in the DC circuit

Definition 2 (Ground Voltage (V_{GND})).

= 0

Definition 3 (Input high (V_{IH}) and Input Low (V_{IL}) of a gate).

V_{IH} is the voltage above which the gate considers the logic level to be "HIGH"

0-5V
minimum

$$V_{IH} = 2.5V$$

$$V_{IL} = 2.5V$$

$$V_{OH} = 5V$$

$$V_{OL} = 0V$$

Definition 4 (Output high (V_{OH}) and Output low (V_{OL}) of gate).

V_{OH} is the voltage that the gate will output for a "1" output


Definition 5 (Positive logic and Negative logic).

fan-out capacity

Definition 6 (Noise margins (NM_L and NM_H) of a channel).

$$NM_H = |V_{OH} - V_{IH}| > 0$$

$$NM_L = |V_{IL} - V_{OL}| > 0$$

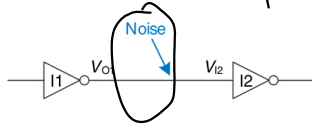

Example 1.

If $V_{DD} = 5V$, $V_{IL} = 1.35V$, $V_{IH} = 3.15V$, $V_{OL} = 0.33V$ and $V_{OH} = 3.84V$ for both the "inverters", then what are the low and high noise margins? Can the circuit tolerate 1V of noise at the channel?

$$NM_H = V_{OH} - V_{IH} = 3.84 - 3.15 = 0.69V$$

$$NM_L = V_{IL} - V_{OL} = 1.35 - 0.33 = 1.02V$$

3 Semiconductors and Doping


Not in syllabus but good to know

Elements recognized as metalloids V·T·E


	13	14	15	16	17
2	B Boron	C Carbon	N Nitrogen	O Oxygen	F Fluorine
3	Al Aluminium	Si Silicon	P Phosphorus	S Sulfur	Cl Chlorine
4	Ga Gallium	Ge Germanium	As Arsenic	Se Selenium	Br Bromine
5	In Indium	Sn Tin	Sb Antimony	Te Tellurium	I Iodine
6	Tl Thallium	Pb Lead	Bi Bismuth	Po Polonium	At Astatine

■ Commonly recognized (86-99%): B, Si, Ge, As, Sb, Te
■ Irregularly recognized (40-49%): Po, At
■ Less commonly recognized (24%): Se
■ Rarely recognized (8-10%): C, Al
 (All other elements cited in less than 6% of sources)
 Arbitrary metal-nonmetal dividing line: between Be and B, Al and Si, Ge and As, Sb and Te, Po and At

Non-metal

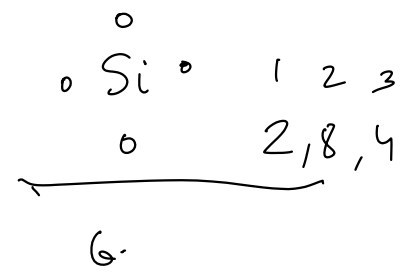


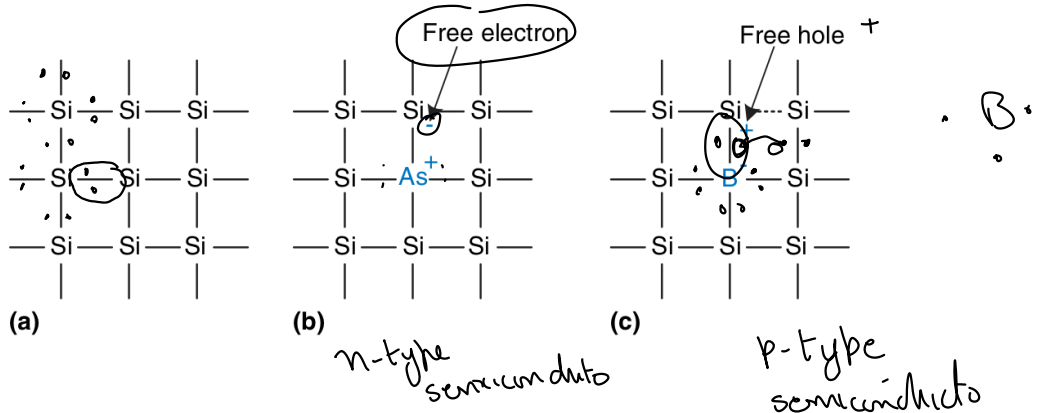Adding impurities → n-type As
 Doping → p-type B





4 MOSFET: Metal Oxide Field Effect Transistors

Not in syllabus but good to know


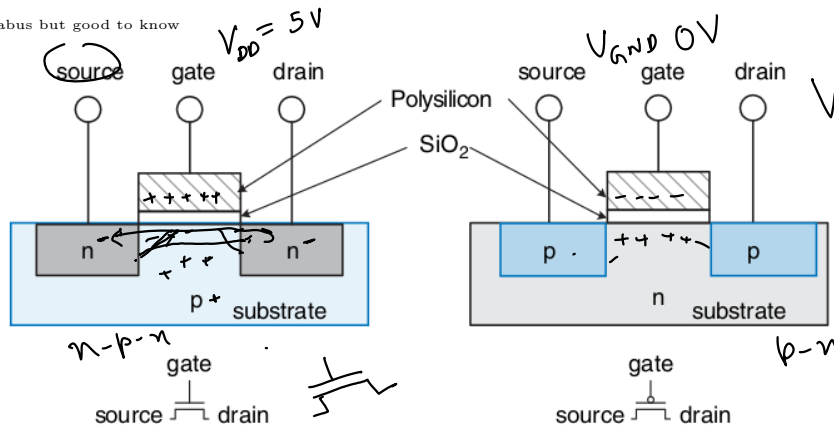


$V_a > (V_t) = 0.7V$
 threshold voltage

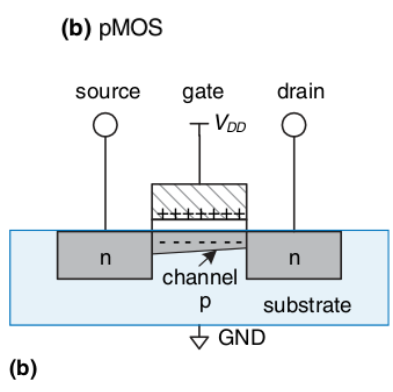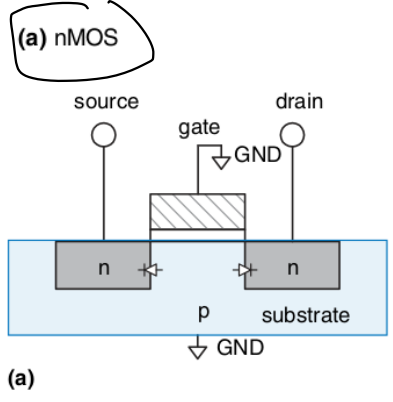


nMOS operation


5 DC Transfer characteristic

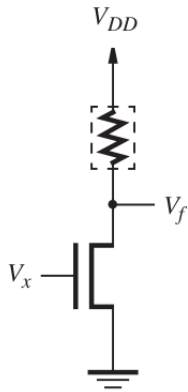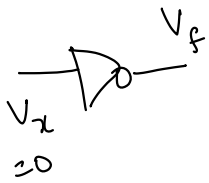

(a) NMOS NOT gate

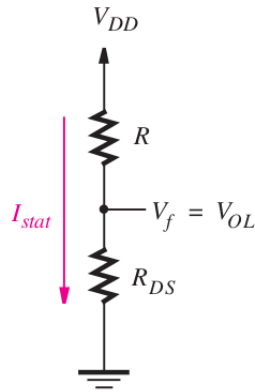


(b) $V_x = 5V$

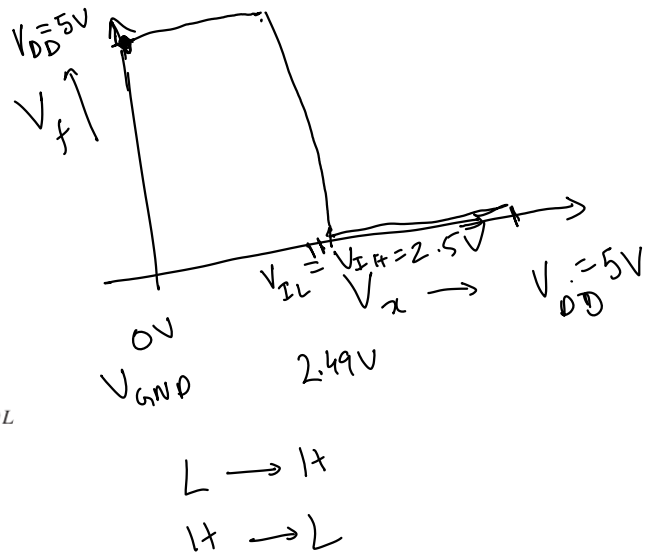


L → H
H → L


$$V_{IL} = V_{IH} = 2.5$$

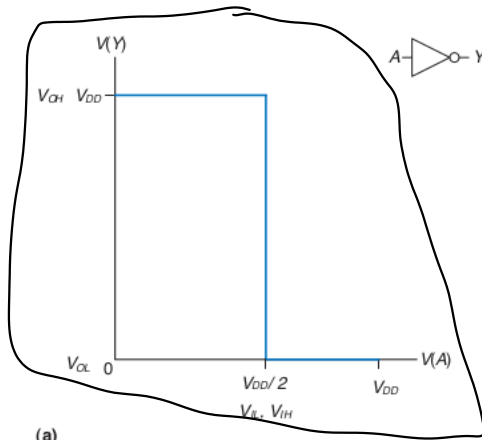


(a)

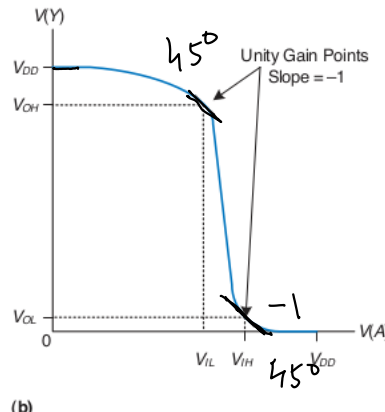


(b)

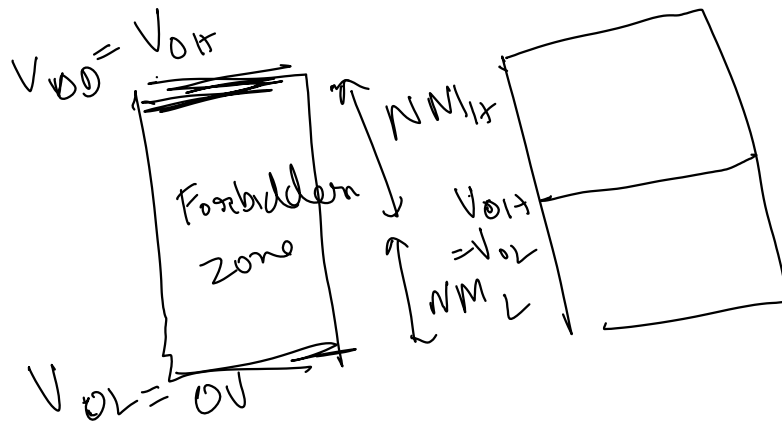


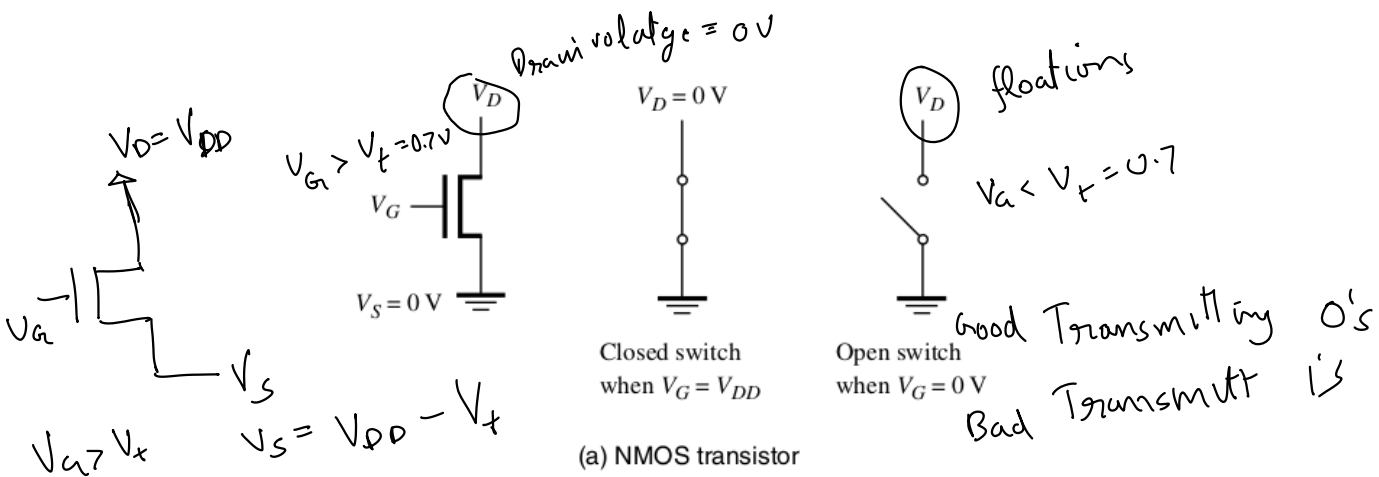


PMOS

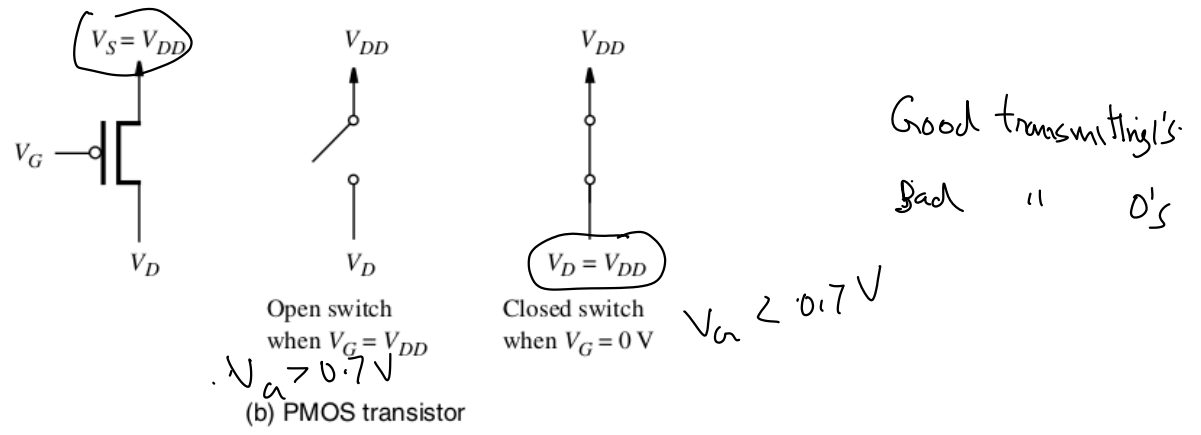

Example 2. Draw a NOT gate using nMOS transistors.

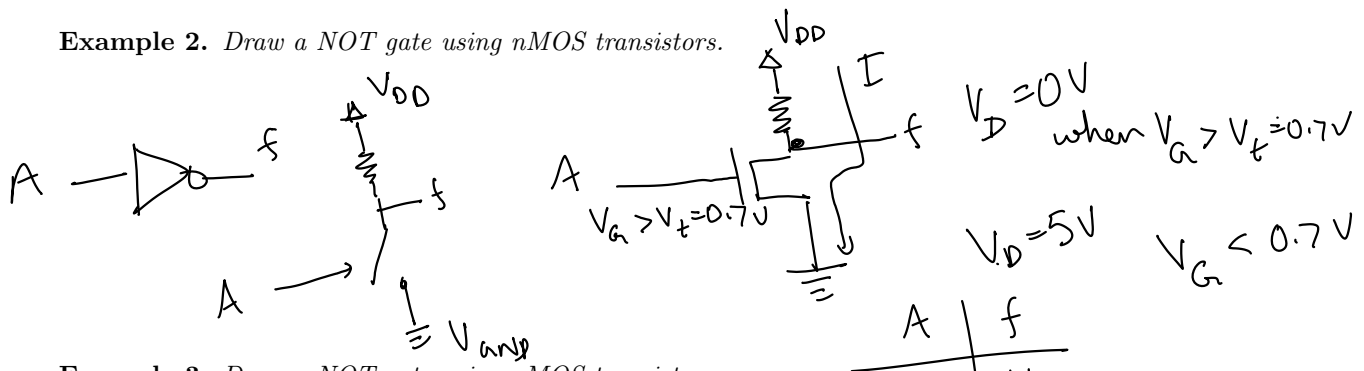

Example 3. Draw a NOT gate using pMOS transistors.

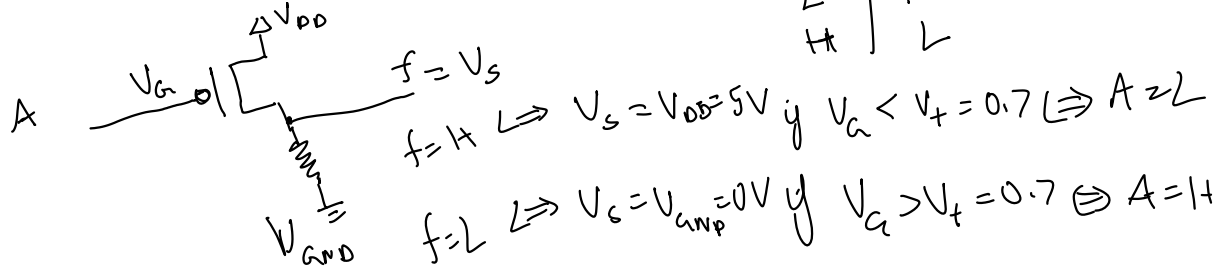


Remark 1. nMOS transistors pass 0's well (output between 0 and $V_{DD} - V_t$). pMOS transistors pass 1's well (output between V_t and V_{DD}).

CMOS - complementary MOS technology

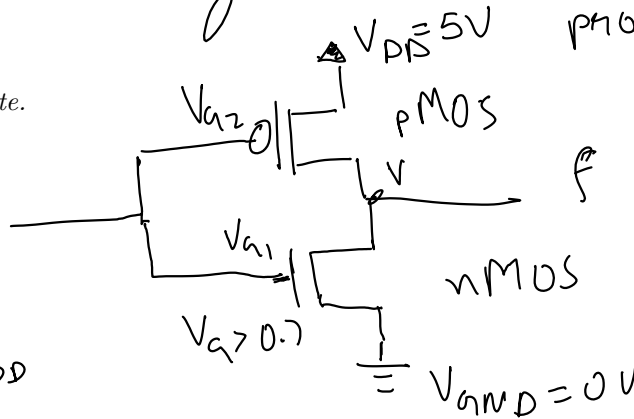Example 4. Draw CMOS NOT Gate.


if $V_A = V_{G1} = V_{G2} < V_t = 0.7V$
 then $V_f = 5V = V_{DD}$




if $V_A > V_t = 0.7V$
 then $V_f = 0V$

Example 5. Draw a two input CMOS NAND Gate

nMOS
NAND

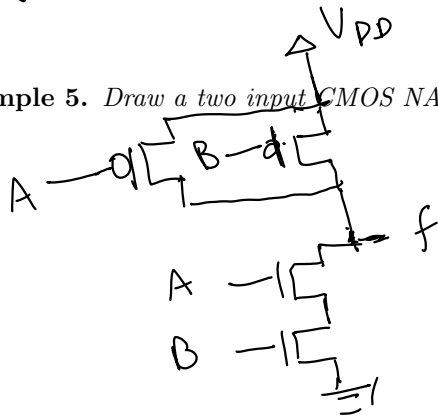

V_A	V_B	V_f
L	L	H
H	L	H
L	H	H
H	H	L

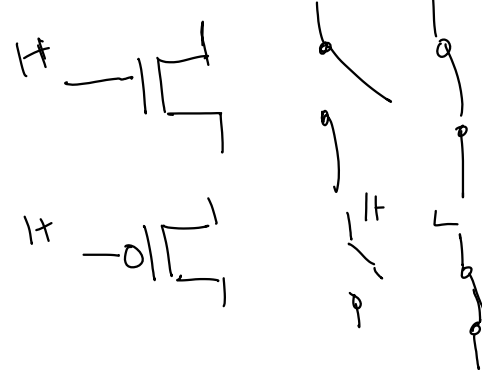

Definition 7 (Negative logic).

Example 6. Analyze the above circuit under negative logic.

Positive logic

$H = 1, L = 0$

Negative logic

$H = 0, L = 1$

V_A	V_B	V_f
L	L	H
L	H	H
H	L	H
H	H	L

Example 7. Draw a three input NAND using CMOS.

Pos Logic
NAND gate


A	B	f
0	0	1
0	1	1
1	0	1
1	1	0

A	B	f
1	1	0
1	0	0
0	1	0
0	0	1


Example 8. Draw a three input NOR using CMOS.

ve logic
NOR gate

PMOS

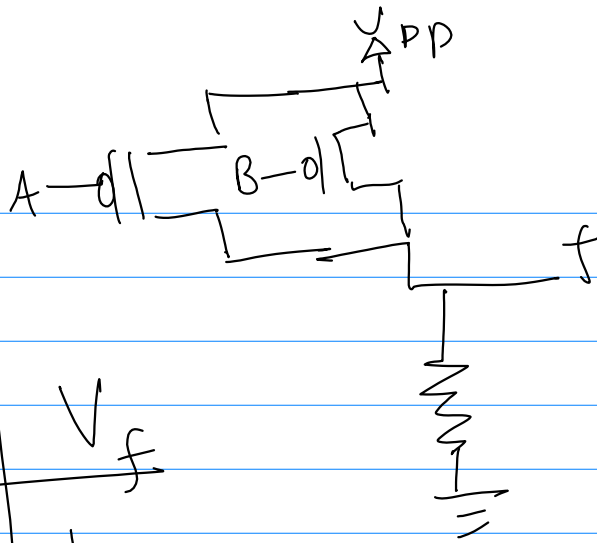

V_A	V_B	V_f
L	L	H
L	H	H
H	L	H
H	H	L

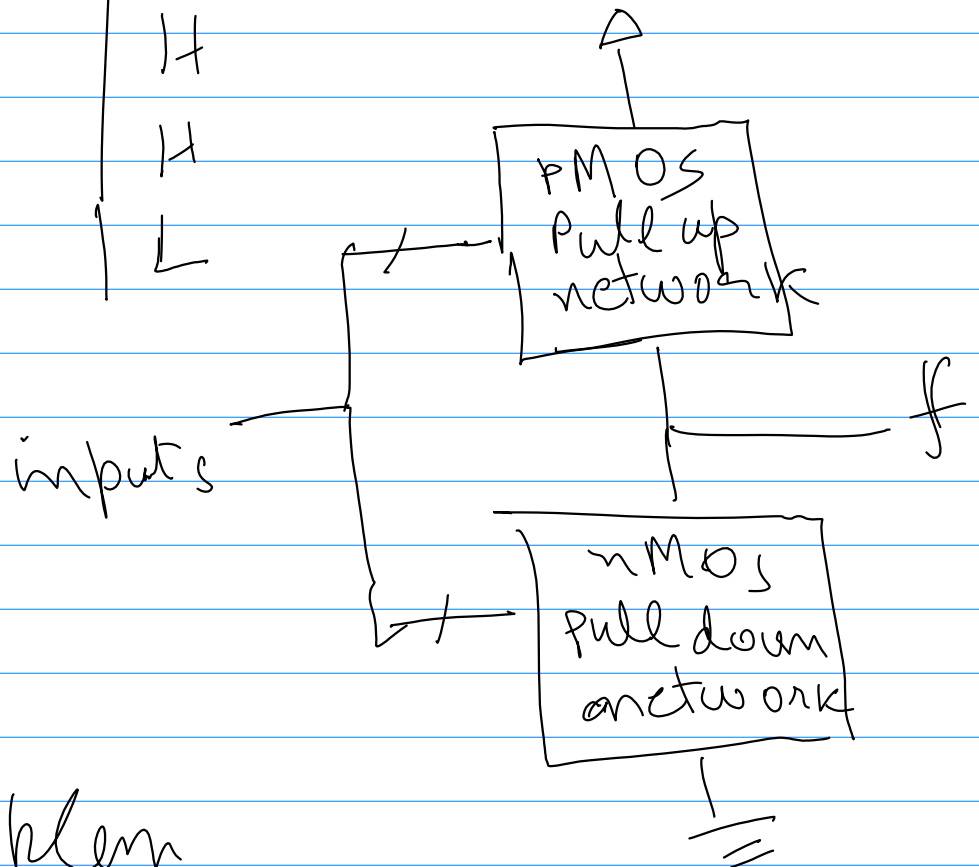


Practice problem

two input NOR gate using CMOS

nMOS

V_A	V_B	V_f
L	L	H
L	H	L
H	L	L
H	H	L

$$V_{DD} - V_t$$

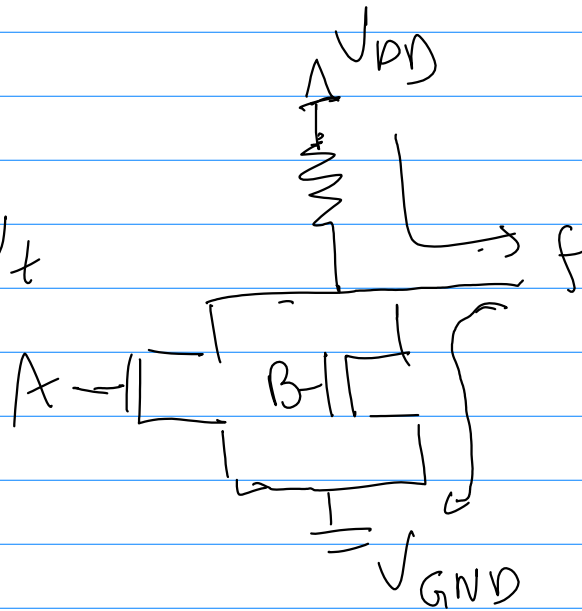


NOR gate

nMOS is bad at transmitting 1's.



pMOS

CMOS NOR gate


V_A	V_B	V_f
L	L	H
L	H	L
H	L	L
H	H	L

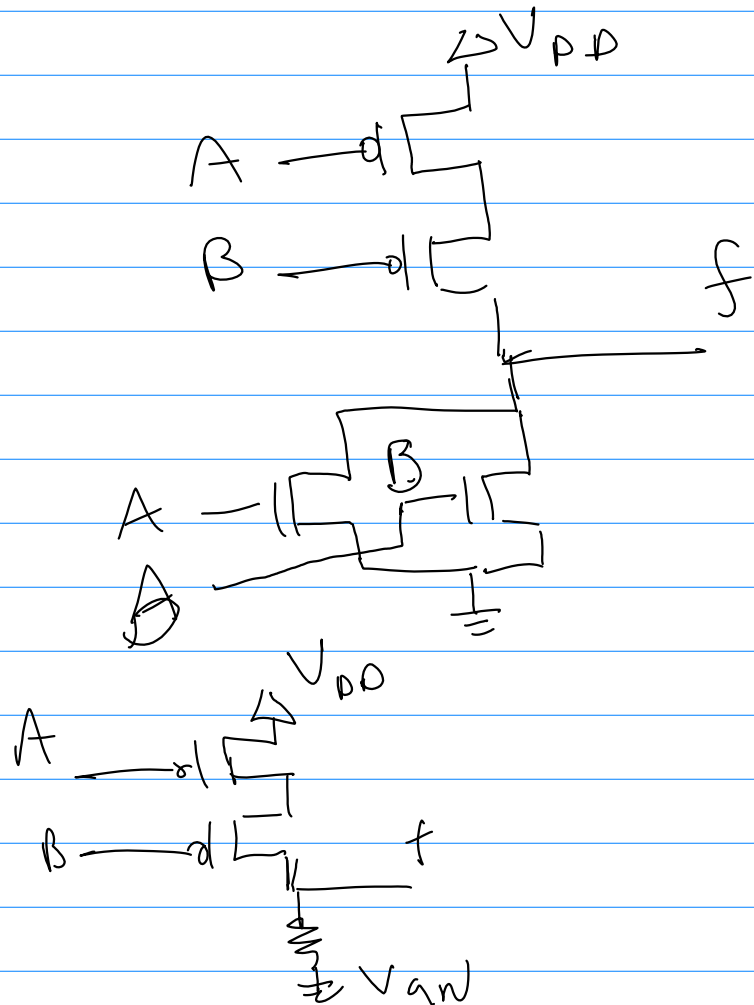


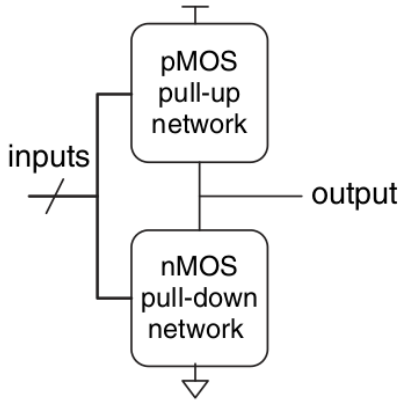
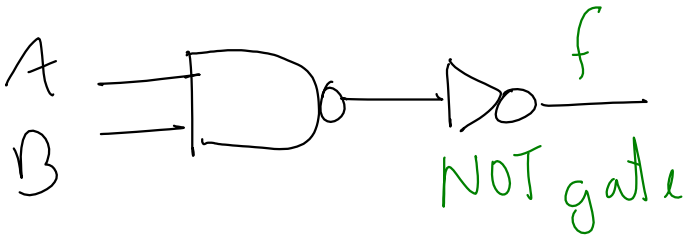
Example 9. Draw a two input AND gate using CMOS.



5.1 Gates with floating output

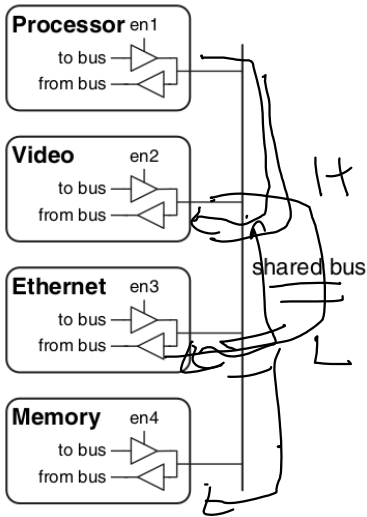

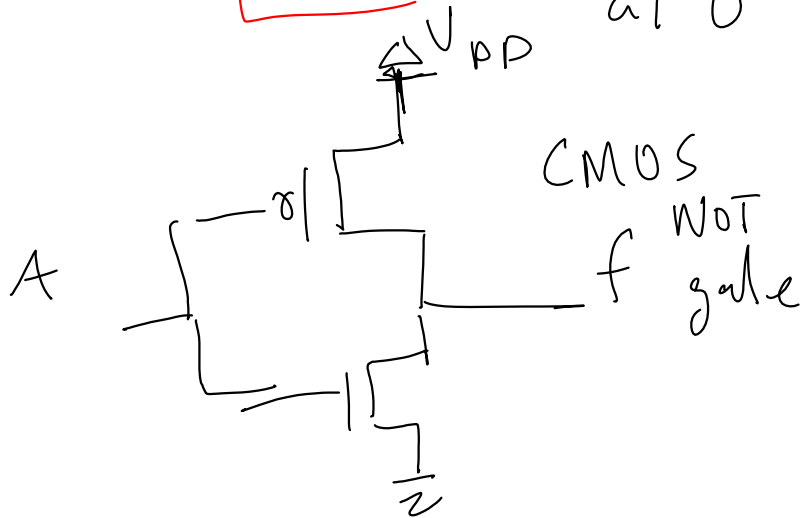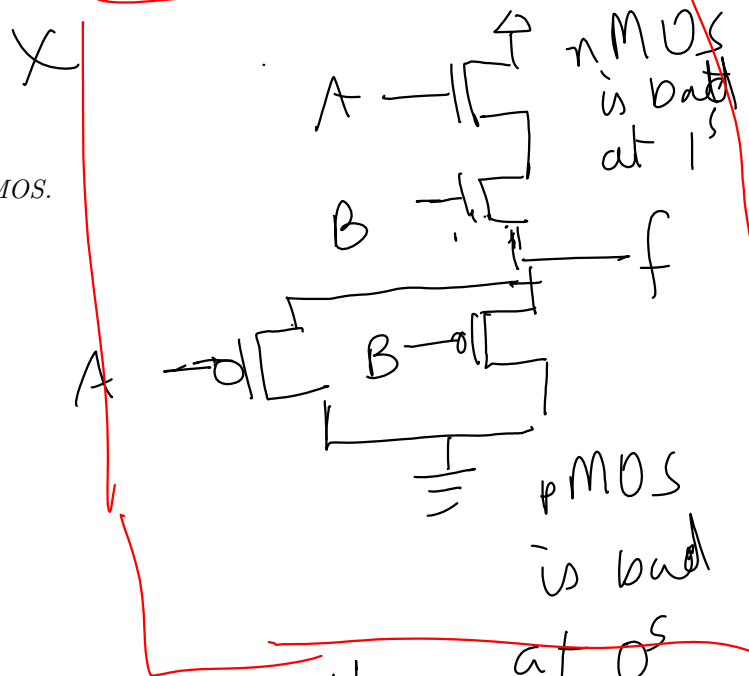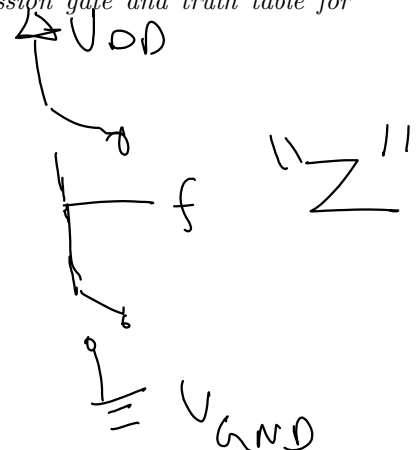Definition 8 (Transmission gate). Draw a schematic of transmission gate and truth table for transmission gate. What is its commonly used symbol?



H and L
and High impedance
state
or floating output

Definition 9 (Tristate buffer). *What is tristate buffer? Draw it's symbol and truth table? Where is it used?*

Example 10. *Draw a Multiplexer using transmission gates.*

Example 11. *Draw a Multiplexer using tristate buffers.*

Definition 10 (Totem-pole). *Draw a Push-pull (or Totem-pole) output NAND gate using CMOS. Can you connect this gate to a shared bus?*

Definition 11 (Tristate). *Draw a Tristate output NAND gate using CMOS with an output enable (OE) input. Can you connect this gate to a shared bus?*

Definition 12 (Open-collector). *Draw a open-collector output NAND gate. Can you connect this gate to a shared bus?*

6 Verilog truth tables

Table 11-11—Bitwise binary AND operator

&	0	1	x	z
0	0	0	0	0
1	0	1	x	x
x	0	x	x	x
z	0	x	x	x


Table 11-12—Bitwise binary OR operator

	0	1	x	z
0	0	1	x	x
1	1	1	1	1
x	x	1	x	x
z	x	1	x	x

7 Timing diagrams and propagation delays

Example 12 (Timing diagram). *Draw a timing diagram for an ideal NAND gate.*


7.1 Delays

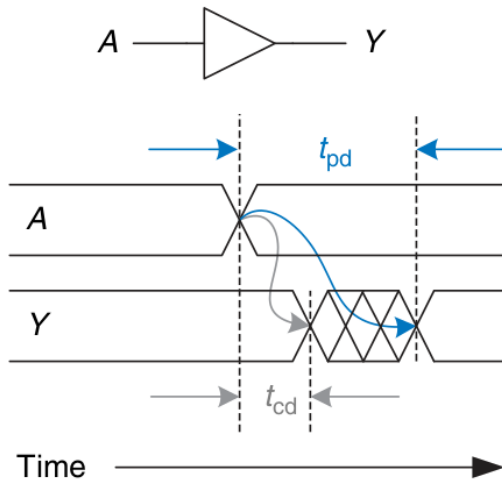

Definition 13 (Propagation delay (t_{pd})).


Definition 14 (Contamination delay (t_{cd})).

7.2 Paths

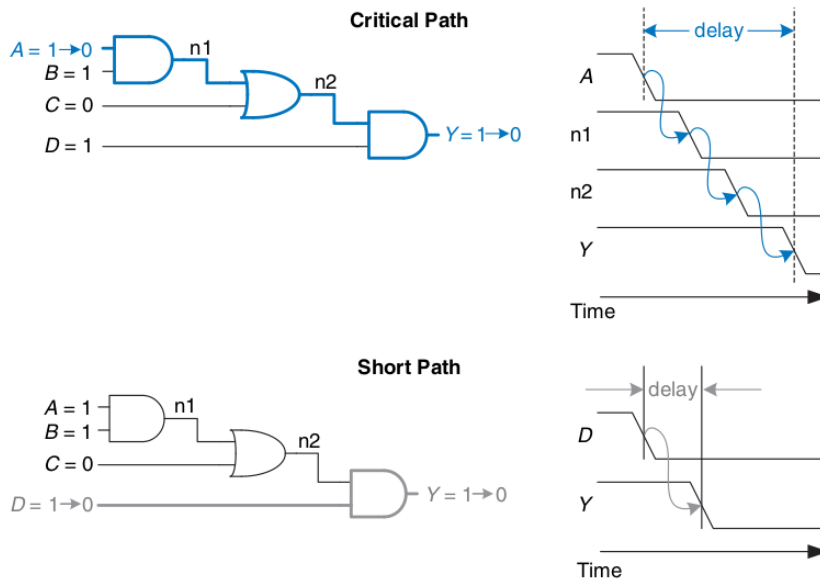

Example 13. Find the propagation delay of the circuit above given that propagation delay of each gate is 100ps add contamination delay of 60ps.

8 Glitches or Hazards

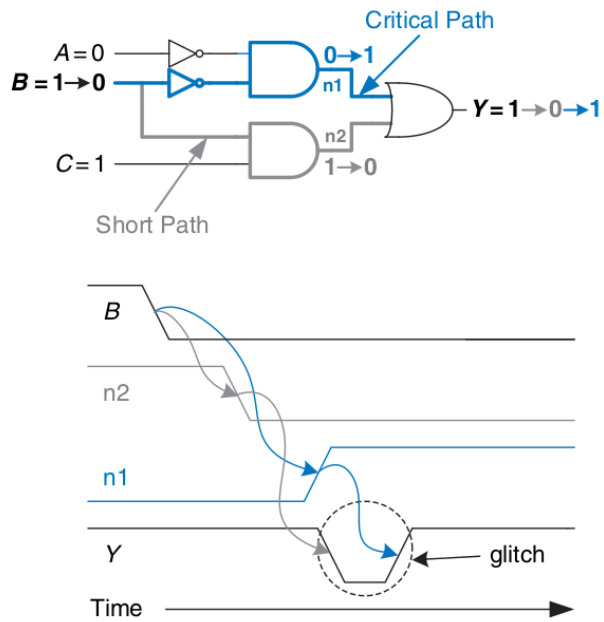

Definition 15 (Glitch or Hazard).

Example 14. Design a circuit that fixes the glitch in the above circuit (also known as glitch-free or hazard-free circuit).