

Sequential logic design

Vikas Dhiman for ECE275

November 21, 2022

1 Objectives

1. Analyse and design both Mealy and Moore sequential circuits with multiple inputs and multiple outputs
2. Convert between Mealy and Moore designs

2 Mealy vs Moore Finite State Machines

Definition 1 (Finite State Machines (FSM)). [1, Sec 3.4]

FSM is another name for sequential circuits.

FSM is defined in opposition to Infinite State Machines (Turing Machines).

Definition 2 (Mealy FSM). [1, Sec 3.4.3]


Mealy FSM have outputs that depend up on both inputs and the state of the circuit or the FSM.

Definition 3 (Moore FSM). [1, Sec 3.4.3]

Moore FSM have outputs that depend only upon the states of the FSM.

Example 1. *A sequential circuit has one input (X) and one output (Z). The circuit examines groups of four consecutive inputs and produces an output $Z=1$ if the input sequence 0010 or 0001 occurs. The sequences can overlap. Draw both Mealy and Moore timing diagrams. Find the Mealy and Moore state graph.*

seq detector

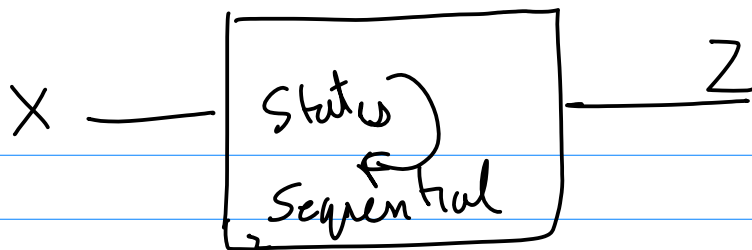

0010 } Z=1
0001 }

otherwise Z=0

X 0 0 0 1 0 0 1 1 0 0 1 0

← Arbitrary example

Mealy output

Z 0 0 0 1 0 0 0 0 0 0 0 1

(states)

Z 0 0 0 0 1 1 0 0 0 0 0 1

Moore output

X 0 0 0 1 0 0 1 1 0 0 1 0

Mealy Z

0 0 0 1 1 0 0 0 0 0 1 1

Moore Z



0 0 0 1 1 0 0 0 0 1 0 0 1 1

Practice Problem 1. *A sequential circuit has one input (X) and one output (Z). The circuit examines groups of four consecutive inputs and produces an output $Z=1$ if the input sequence 0101 or 1001 occurs. The circuit resets after every four inputs. Draw both Mealy and Moore timing diagrams. Find the Mealy and Moore state graph.*

Inputs


References

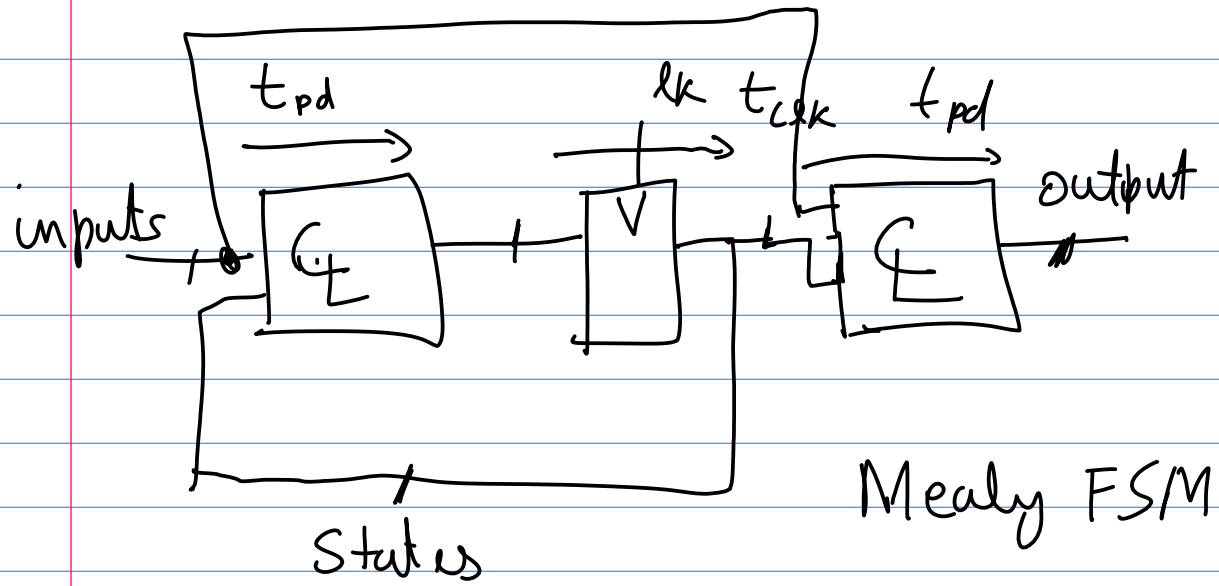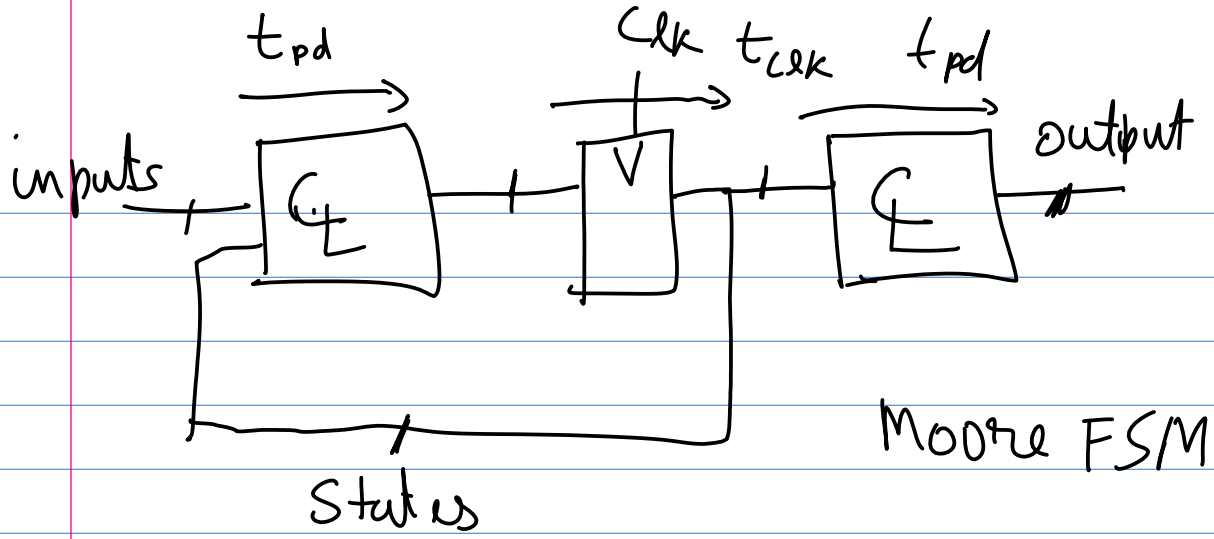- [1] Sarah L Harris and David Harris. *Digital design and computer architecture*. Morgan Kaufmann, 2022.




X	0	0	0	1	0	0	1	1	0	0	1	0	← Arb. n example
Mealy output Z	0	0	0	1	0	0	0	0	0	0	0	1	
Moore output Z	0	0	0	0	1	1	0	0	0	0	0	1	

Mealy state diagrams

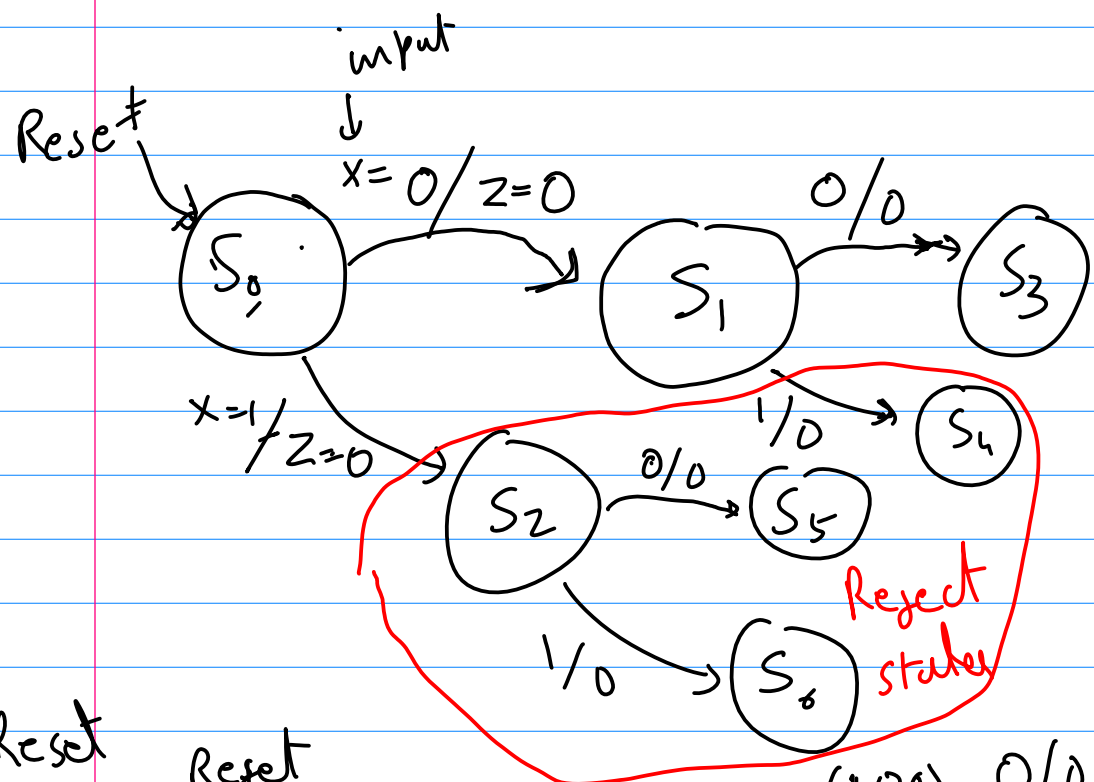

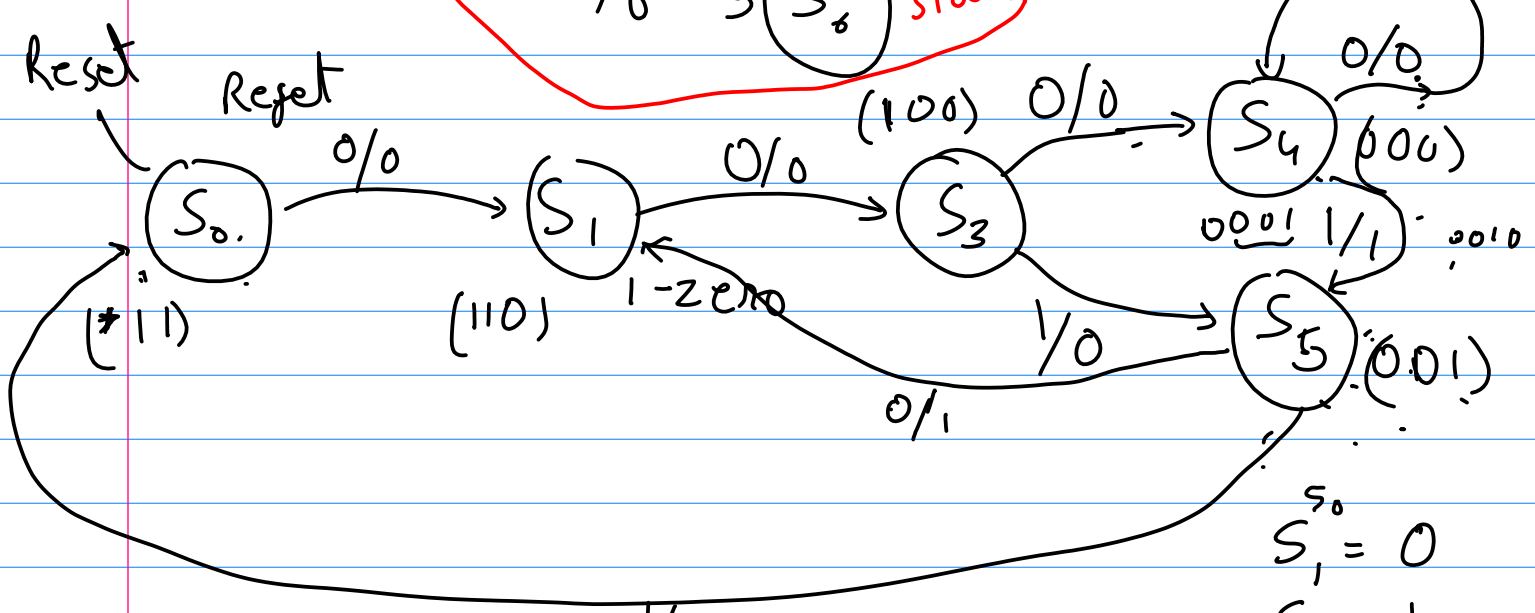- $S_0 = \overline{0010}$
 $S_1 = 0$
 $S_2 = 1$
 $S_3 = 00$
 $S_4 = 01$
 $S_5 = 10$
 $S_6 = 11$



5 - states # FF = 3

- $S_0 = 0010$
 $S_1 = 0$
 $S_2 = 1$
 $S_3 = 00$
 $S_4 = 000$
 $S_5 = 001$

$$\begin{array}{l} L_2 C_0 \\ S_0 = 000 \\ S_1 = 001 \\ S_3 = 011 \\ S_4 = 100 \\ S_5 = 101 \end{array}$$