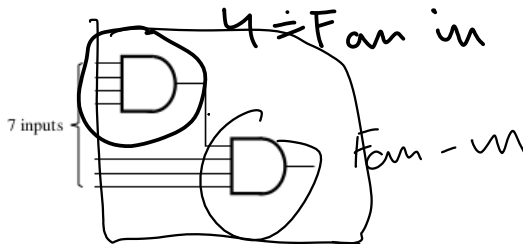


Sequential logic design: More terminology

Vikas Dhiman for ECE275

December 7, 2022


Definition 1 (Fan-in). The fan-in of a logic gate is number of inputs to a logic gate. [2, Section B.8.9]





Remark 1 (Fan-in). The fan-in of a gate is limited by the propagation delay t_p . Higher the fan-in, higher the t_p . The output voltage thresholds like V_{OL} and V_{OH} also limit fan-in. Higher the fan-in, higher is V_{OL} (and lower is the V_{OH}).

Example 1. Implement an OR gate with fan-in of 7 using OR gates with fan-in of 3.

$$(A) + (B + C + D) + (E + F + G)$$

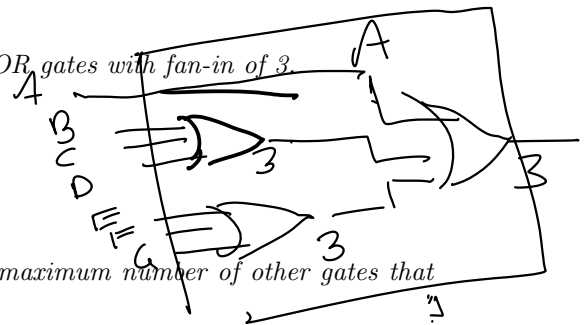


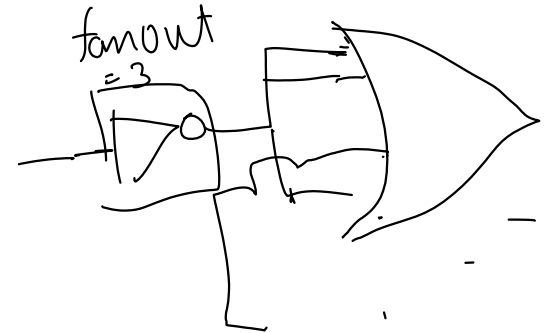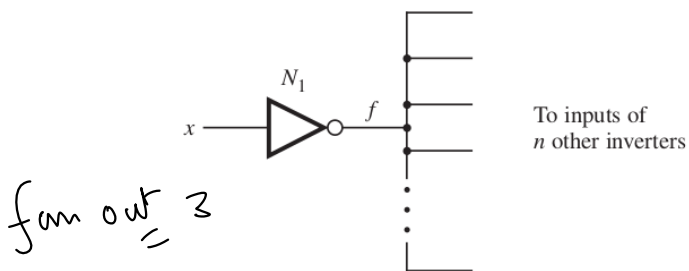Definition 2 (Fan-out). The fan-out of a logic gate is the maximum number of other gates that can be connected to output of a gate. [2, Section B.8.9]



Definition 3 (Programmable Logic Array (PLA)). Structure of a PLA:

AND-OR PLA

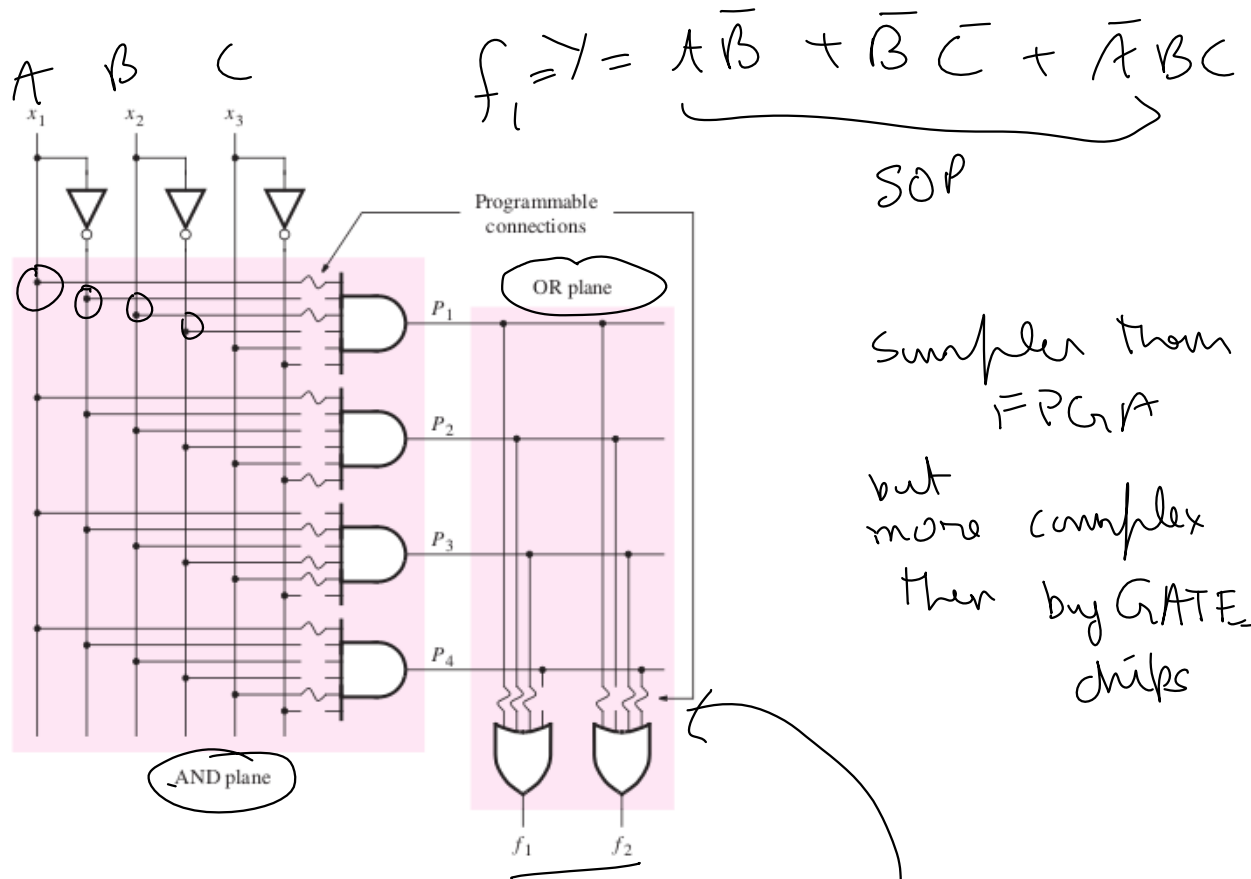

Simple than
FPGA
but
more complex
than
big GATES
chips

Figure B.26 Gate-level diagram of a PLA.

[2, Section B.6.1]

Definition 4 (Programmable Array Logic (PAL)). Structure of a PAL:


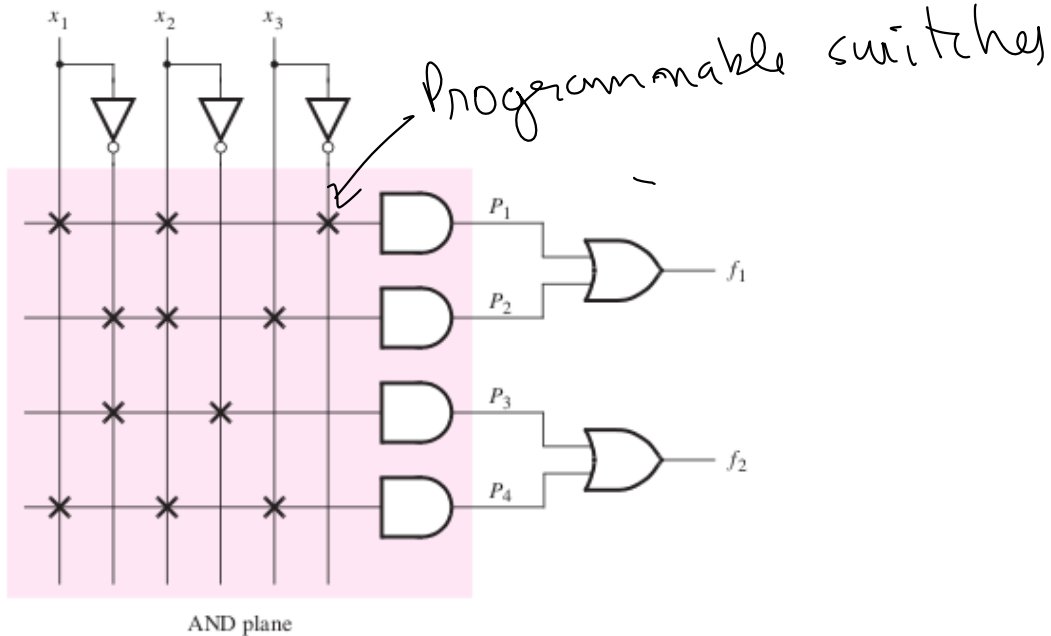


Figure B.28 An example of a PAL.

[2, Section B.6.2]

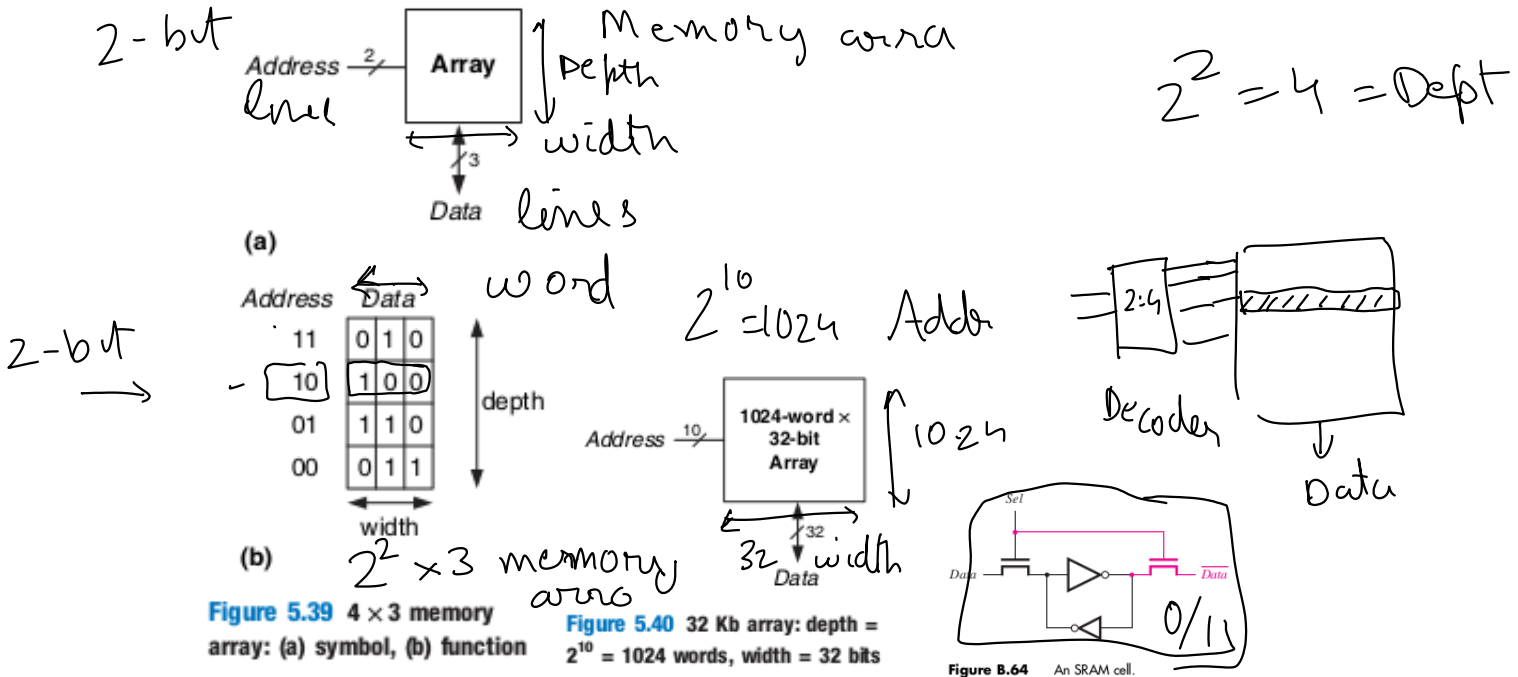Example 2. What is the difference between PLA and PAL?

Definition 5 (Random Access Memory (RAM)). Structure of a RAM is as follows:



RAM

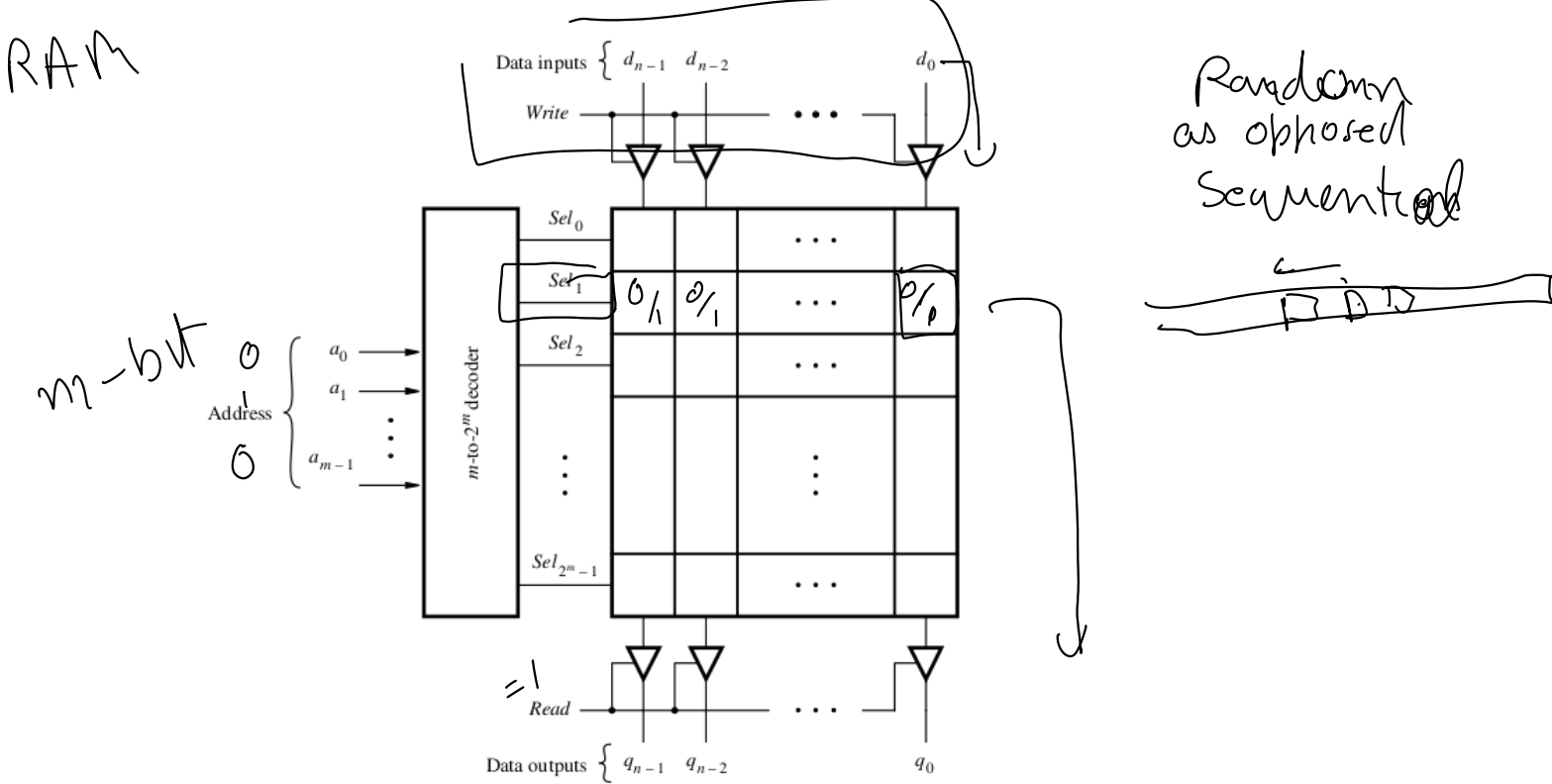


Figure B.66 A $2^m \times n$ SRAM block.

Definition 6 (Read Only Memory (ROM)). Structure of a ROM is as follows:



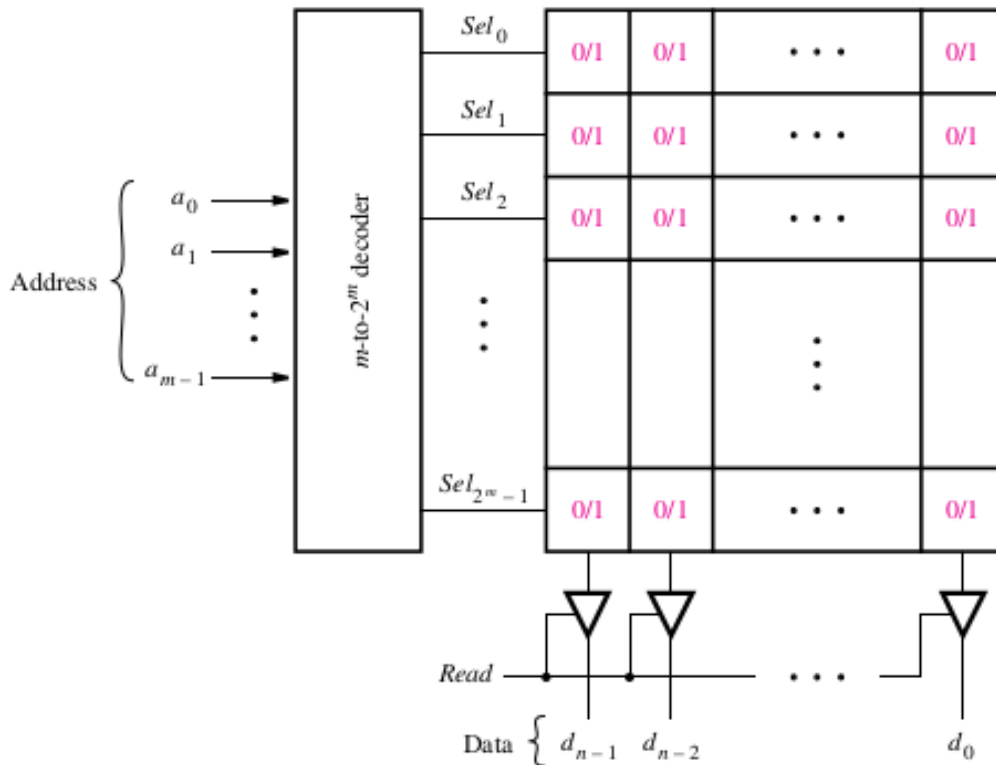


Figure B.72 A $2^m \times n$ read-only memory (ROM) block.

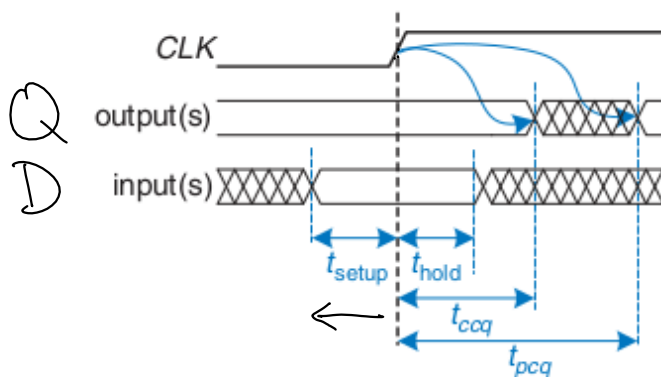1 Timing parameters for sequential circuit [1, Section 3.5]



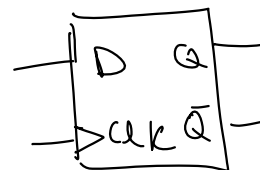t_p = prop delay
 t_c = contamination delay



t_{ccq} = clock to Q contamination delay
 t_{pcq} = clock to Q propagation delay


Definition 7 (Setup time t_{su} of a latch/flip-flop). Time for which input must be stable before the clock edge.

Definition 8 (Hold time t_h of a latch/flip-flop). Time for which input must be stable after the clock edge.

Definition 9 (Clock-to-Q contamination delay t_{ccq} of a latch/flip-flop). Time taken to influence (contaminate) the Q output after the clock edge.

Definition 10 (Clock-to-Q propagation delay t_{ccq} of a latch/flip-flop). Time taken for Q output to stabilize after the clock edge.

2 FPGA [2, Section B.6.5]

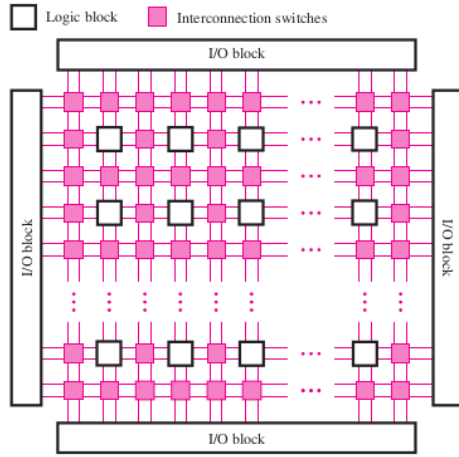

(a) General structure of an FPGA

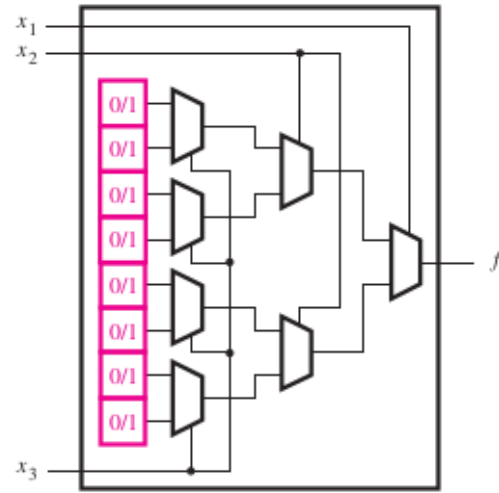


Figure B.37 A three-input LUT.

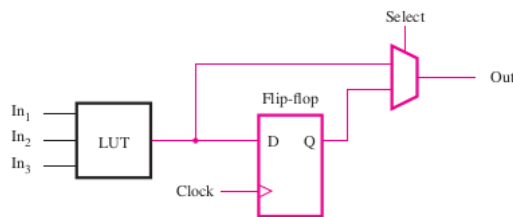


Figure B.38 Inclusion of a flip-flop in an FPGA logic element.

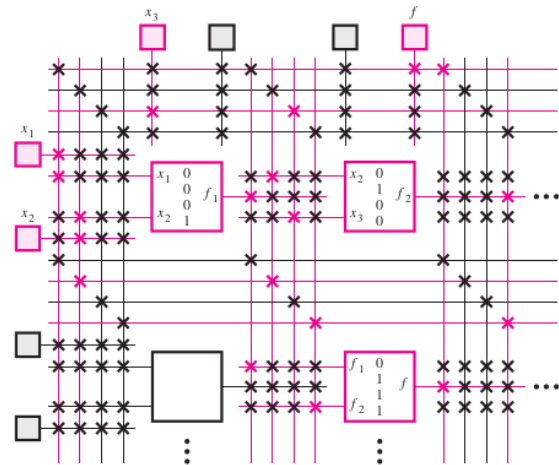


Figure B.39 A section of a programmed FPGA.

References

- [1] Sarah L Harris and David Harris. *Digital design and computer architecture*. Morgan Kaufmann, 2022.
- [2] Brown Stephen and Vranesic Zvonko. *Fundamentals of digital Logic with Verilog design*. McGraw Hill, 2022.