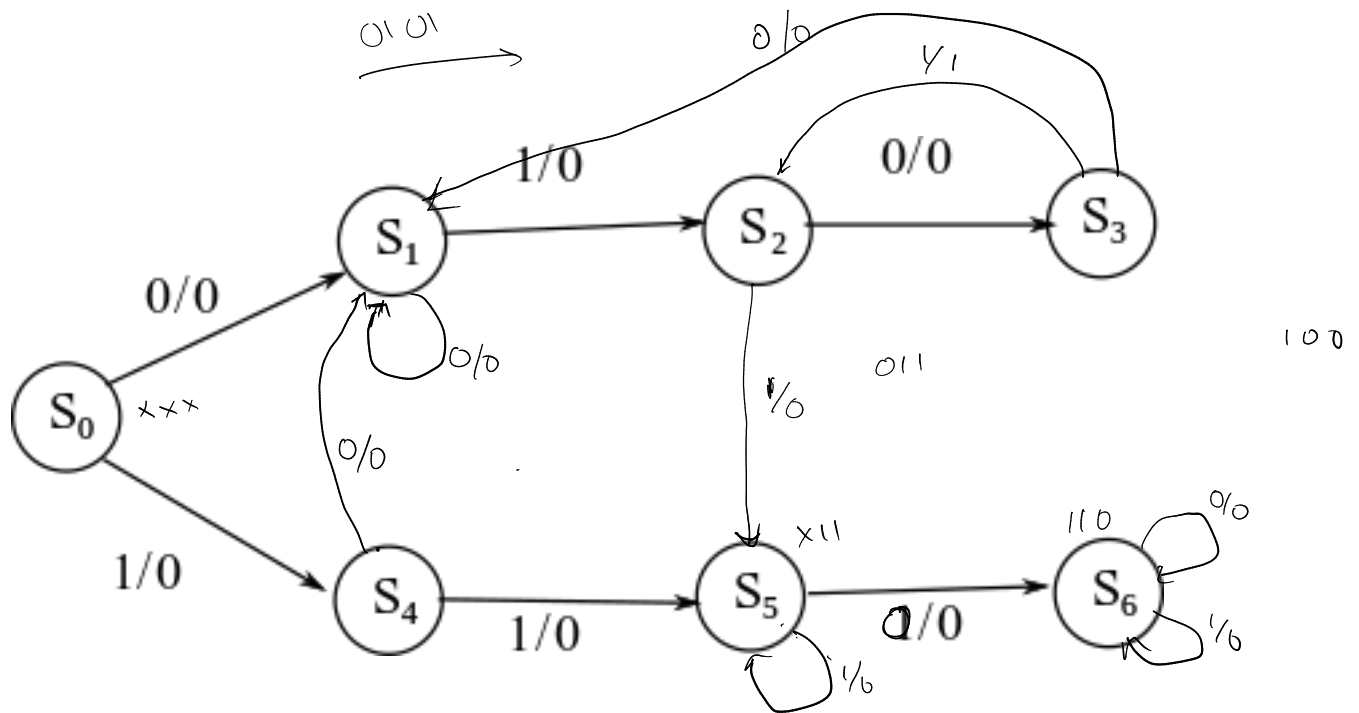


Problem 1. Complete the following state diagram. You can also choose to draw state diagram from scratch. Also fill the state transition table. (20 marks)

State	Meaning
S ₀	xxx
S ₁	xx0
S ₂	x01
S ₃	"010"
S ₄	xx1
S ₅	x11
S ₆	"110"

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S ₀	S ₁	S ₄	0	0
S ₁	S ₁	S ₂	0	0
S ₂	S ₃	S ₅	0	0
S ₃	S ₁	S ₂	0	1
S ₄	S ₁	S ₅	0	0
S ₅	S ₆	S ₅	0	0
S ₆	S ₆	S ₆	0	0



Problem 2. Can the above state table be reduced? Find
 Only specify which states are equivalent to each other
 the state table again. (10 marks)

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S ₀	S ₁	S ₄		0
S ₁	S ₁	S ₂	0	0
S ₂	S ₃	S ₃	0	0
S ₃	S ₁	S ₂	0	1
S ₄	S ₁	S ₅	0	0
S ₅	S ₅	S ₅	0	0
S ₆	S ₅	S ₆	0	0

S ₀							
S ₁	2=4						
S ₂	1=3 4=5	1=3 2=4					
S ₃	X	X	X				
S ₄	1=3 2=5	2=5	1=3 2=5	X			
S ₅	1=3 4=5	1=3 5=6	3=6	X	1=3		
S ₆	1=3 4=5	5=6 2=5	6=3 6=5	X	6=3 6=5	5=6 ✓	
	S ₀	S ₁	S ₂	S ₃	S ₄	S ₅	S ₆

$$S_5 \equiv S_6$$

Problem 3. (State assignment).

Using the guideline method find the groups of states that should be grouped together. Draw the state assignment map. Assign a 3-bit state encoding to the states in the reduced state table derived in Problem 2. (20 marks).

Present State	Next State		Output	
	X=0	X=1	X=0	X=1
S ₀	S ₁	S ₄	0	0
S ₁	S ₁	S ₂	0	0
S ₂	S ₃	S ₅	0	0
S ₃	S ₁	S ₂	0	0
S ₄	S ₁	S ₅	0	0
S ₅	S ₅ → S ₅	S ₅	0	0
S ₆	S ₆	S ₆	0	0

$G_1: (S_0, S_1, S_3, S_4), (S_1, S_3), (S_2, S_4, S_5)$

$G_2: (S_1, S_4), (S_1, S_2), (S_3, S_5), (S_4, S_5)$

	y_2				
	0	2	6	4	
y_0	S ₀	S ₁	S ₄	S ₃	S ₀
	1	S ₂	S ₅	5	S ₁
					S ₂
					S ₃
					S ₄
					S ₅

	y_2	y_1	y_0
S ₀	0	0	0
S ₁	0	1	0
S ₂	0	1	1
S ₃	1	0	0
S ₄	1	1	0
S ₅	1	1	1

Problem 4. The following state-assigned table is given. Find the boolean expressions for inputs J_1 and K_1 to a J-K flip flop that implements the transition from Present state y_1 to Next state Y_1 . Express the inputs J_1 and K_1 in terms of input X and present state y_2, y_1 and y_0 (20 marks).

Present state			Next State						Output	
y_2	y_1	y_0	$X=0$			$X=1$			$X=0$	$X=1$
			Y_2	Y_1	Y_0	Y_2	Y_1	Y_0		
0	0	0	0	0	1	0	0	0	0	0
0	0	1	1	1	1	0	1	1	1	1
0	1	0	0	1	1	1	0	0	0	0
0	1	1	0	1	1	1	1	1	1	0
1	0	0	d	d	d	d	d	d	d	d
1	0	1	1	1	0	1	1	1	1	0
1	1	0	1	0	0	1	0	0	1	0
1	1	1	1	1	0	1	1	1	1	0

J_1

y_2	y_1	y_0	J_1
0	0	0	d
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	d
1	0	1	1
1	1	0	1
1	1	1	1

y_2	y_1	J_1	K_1
0	0	0	d
0	1	1	d
1	0	d	1
1	1	d	0

$J_1 = xy_0 + \bar{x}\bar{y}_2$

y_2	y_1	y_0	J_1
0	0	0	d
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	d
1	0	1	1
1	1	0	1
1	1	1	1

K_1

y_2	y_1	y_0	K_1
0	0	0	d
0	0	1	d
0	1	0	d
0	1	1	d
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

$\bar{K}_1 = y_0 + \bar{x}\bar{y}_2$
 $\Rightarrow K_1 = \bar{y}_0(x + y_2)$

