

Homework 2 solution

Max marks: 110

Due on September 17, 2021, 9 AM, before class.

| Row | x_1 | x_2 | x_3 | f |
|-----|-------|-------|-------|-----|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 1 |
| 3 | 0 | 1 | 1 | 0 |
| 4 | 1 | 0 | 0 | 1 |
| 5 | 1 | 0 | 1 | 0 |
| 6 | 1 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 1 |

Table 1: Truth table for a 3-way light switch

1 Sept 10th Lecture

Problem 1 If the SOP form for $\bar{f} = A\bar{B}\bar{C} + \bar{A}\bar{B}$, then give the POS form for f . [10 marks]

Solution

Take inversion on both sides

$$\begin{aligned} \bar{\bar{f}} &= \overline{A\bar{B}\bar{C} + \bar{A}\bar{B}} \\ f &= \overline{A\bar{B}\bar{C}} \cdot \overline{\bar{A}\bar{B}} && \text{by DeMorgan's} \\ &= (\bar{A} + B + C)(A + B) && \text{by DeMorgan's} \end{aligned}$$

Problem 2 Use DeMorgan's Theorem to find f if $\bar{f} = (A + BC)D + EF$. [10 marks]

Solution

Take inversion on both sides

$$\begin{aligned} \bar{\bar{f}} &= \overline{(A + BC)D + EF} \\ f &= \overline{((A + BC)D)} \cdot \overline{EF} && \text{by DeMorgan's} \\ &= (\overline{(A + BC)} + \bar{D})(\bar{E} + \bar{F}) && \text{by DeMorgan's} \\ &= (\bar{A}(\bar{B}\bar{C}) + \bar{D})(\bar{E} + \bar{F}) && \text{by DeMorgan's} \\ &= (\bar{A}(\bar{B} + \bar{C}) + \bar{D})(\bar{E} + \bar{F}) && \text{by DeMorgan's} \end{aligned}$$

Problem 3 Implement the function in Table 1 using only NAND gates. [10 marks]


Solution

To implement the function using NAND gates, we seek the SOP form of the function,

| | \bar{x}_1 | x_1 | | |
|-------------|-------------|-------------|---|---|
| \bar{x}_2 | x_2 | \bar{x}_2 | | |
| \bar{x}_3 | 0 | 1 | 0 | 1 |
| x_3 | 1 | 0 | 1 | 0 |

The function cannot be simplified beyond minterms.
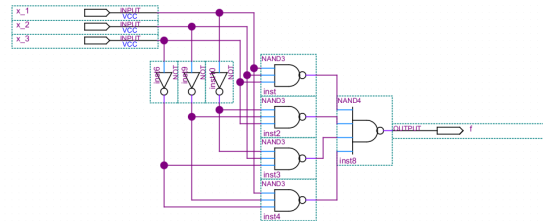
$$\begin{aligned} f &= \bar{x}_1\bar{x}_2x_3 + \bar{x}_1x_2\bar{x}_3 + x_1\bar{x}_2\bar{x}_3 + x_1x_2x_3 \\ &= \overline{\bar{x}_1\bar{x}_2x_3} + \overline{\bar{x}_1x_2\bar{x}_3} + \overline{x_1\bar{x}_2\bar{x}_3} + \overline{x_1x_2x_3} \\ &= \overline{\bar{x}_1\bar{x}_2x_3} \cdot \overline{\bar{x}_1x_2\bar{x}_3} \cdot \overline{x_1\bar{x}_2\bar{x}_3} \cdot \overline{x_1x_2x_3} \end{aligned}$$



Problem 4 Implement the function in Table 1 using only NOR gates. [10 marks]

Solution

To implement the function using NAND gates, we seek the POS form of the function. We plot the K-map for \bar{f} ,

| | \bar{x}_1 | x_1 | | |
|-------------|-------------|-------------|---|---|
| \bar{x}_2 | x_2 | \bar{x}_2 | | |
| \bar{x}_3 | 1 | 0 | 1 | 0 |
| x_3 | 0 | 1 | 0 | 1 |

The function \bar{f} cannot be simplified further,


$$\bar{f} = \bar{x}_1\bar{x}_2\bar{x}_3 + \bar{x}_1\bar{x}_2x_3 + \bar{x}_1x_2\bar{x}_3 + x_1\bar{x}_2x_3$$

Taking inverse of both sides and observing $\bar{\bar{f}} = f$.

$$\begin{aligned} f &= (x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + x_3) \\ &= \overline{(x_1 + x_2 + x_3)(x_1 + \bar{x}_2 + \bar{x}_3)(\bar{x}_1 + x_2 + \bar{x}_3)(\bar{x}_1 + \bar{x}_2 + x_3)} \end{aligned}$$

$$= (\overline{x_1 + x_2 + x_3}) + (\overline{x_1 + \bar{x}_2 + \bar{x}_3}) + (\overline{\bar{x}_1 + x_2 + \bar{x}_3}) + (\overline{\bar{x}_1 + \bar{x}_2 + x_3})$$

Solution

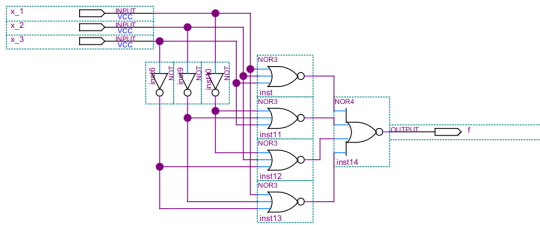

Minimum cost SOP

| | \bar{x}_1 | x_1 |
|-------------|-------------|-------------|
| \bar{x}_2 | x_2 | \bar{x}_2 |
| \bar{x}_3 | 0 | d |
| x_3 | 1 | 0 |

$$f = x_1\bar{x}_2 + x_1x_3 + \bar{x}_2x_3 \quad (4)$$

Cost = 3 AND + 1 OR + (3 * (2 input per AND gate) + 3 inputs per OR gate) inputs = 13

To find minimum cost POS, we draw K-map for \bar{f} ,

| | \bar{x}_1 | x_1 |
|-------------|-------------|-------------|
| \bar{x}_2 | x_2 | \bar{x}_2 |
| \bar{x}_3 | 1 | d + d + d |
| x_3 | 0 | 1 |

$$\bar{f} = \bar{x}_1\bar{x}_3 + \bar{x}_1x_2 + x_2\bar{x}_3 \quad (5)$$

$$\Rightarrow f = (x_1 + x_3)(x_1 + \bar{x}_2)(\bar{x}_2 + x_3) \quad (6)$$

Cost = 3 OR + 1 AND + (3*(2 inputs per OR gate)+3 inputs per AND gate) inputs = 13

2 Sept 13th Lecture

Problem 5 Find the minimum-cost SOP and POS forms for the function $f(x_1, x_2, x_3) = m(1, 2, 3, 5)$. [1, Prob 2.37] [10 marks]

Solution

Minimum cost SOP

| | \bar{x}_1 | x_1 |
|-------------|-------------|-------------|
| \bar{x}_2 | x_2 | \bar{x}_2 |
| \bar{x}_3 | 0 | 1 |
| x_3 | 1 | 1 |

$$f = \bar{x}_1x_2 + \bar{x}_2x_3 \quad (1)$$

Cost = 2 AND + 1 OR + (2 * (2 input per AND gates) + 2 input per OR gate) inputs = 9

To find Minimum cost POS, we draw K-map for \bar{f} .

| | \bar{x}_1 | x_1 |
|-------------|-------------|-------------|
| \bar{x}_2 | x_2 | \bar{x}_2 |
| \bar{x}_3 | 0 | 1 |
| x_3 | 1 | 1 |

$$\bar{f} = \bar{x}_2\bar{x}_3 + x_1x_2 \quad (2)$$

$$\Rightarrow f = (x_2 + x_3)(\bar{x}_1 + \bar{x}_2) \quad (3)$$

Cost = 2 OR + 1 AND + (2 * (2 inputs per OR gate) + 2 input AND gate) inputs = 9

Problem 6 Find the minimum-cost SOP and POS forms for the function $f(x_1, x_2, x_3) = \sum m(1, 4, 7) + D(2, 5)$. [1, Prob 2.38] [10 marks]

Problem 7 Find the minimum-cost SOP and POS forms for the function $f(x_1, x_2, x_3, x_4) = \prod M(0, 1, 2, 4, 5, 7, 8, 9, 10, 12, 14, 15)$. [1, Prob 2.39] [10 marks]

Solution

The function f is zero at the maxterms. We draw the following K-map,

| | \bar{x}_1 | x_1 |
|-------------|-------------|-------------|
| \bar{x}_2 | x_2 | \bar{x}_2 |
| \bar{x}_3 | \bar{x}_4 | 0 |
| x_3 | x_4 | 1 |

$$f = \bar{x}_2x_3x_4 + \bar{x}_1x_2x_3\bar{x}_4 + x_1x_2\bar{x}_3x_4 \quad (7)$$

Cost = 3 AND gates + 1 OR gate + (3+4+4 inputs to the AND gates + 3 inputs to the OR gate) = 18.

To find the POS form, we draw K-map for \bar{f} ,

| | | \bar{x}_1 | | x_1 | |
|-------------|-------------|-------------|-------|-------------|-------|
| | | \bar{x}_2 | x_2 | \bar{x}_2 | x_2 |
| \bar{x}_3 | \bar{x}_4 | 1 + 1 | 1 + 1 | 1 | 1 + 1 |
| | x_4 | 1 | 1 | 0 | 1 |
| x_3 | x_4 | 0 | 1 | 1 | 0 |
| | \bar{x}_4 | 1 | 0 | 1 | 1 + 1 |

$$\begin{aligned}\bar{f} &= \bar{x}_1\bar{x}_3 + \bar{x}_3\bar{x}_4 + x_2x_3x_4 + x_1\bar{x}_2\bar{x}_3 \\ &\quad + x_1x_3\bar{x}_4 + \bar{x}_2x_3\bar{x}_4 \\ \Rightarrow f &= (x_1 + x_3)(x_3 + x_4)(x_2 + x_3 + x_4) \\ &\quad (\bar{x}_1 + x_2 + x_3)\end{aligned}$$

Problem 8 Find the minimum-cost SOP and POS forms for the function $f(x_1, x_2, x_3, x_4) = \sum m(0, 2, 8, 9, 12, 15) + D(1, 3, 6, 7)$. [1, Prob 2.40] [10 marks]

Solution

The K-map for f is

| | | \bar{x}_1 | | x_1 | |
|-------------|-------------|-------------|-------|-------------|-------|
| | | \bar{x}_2 | x_2 | \bar{x}_2 | x_2 |
| \bar{x}_3 | \bar{x}_4 | 1 | 0 | 1 | 1 + 1 |
| | x_4 | d | 0 | 0 | 1 |
| x_3 | x_4 | d | d | 1 | 0 |
| | \bar{x}_4 | 1 | d | 0 | 0 |

$$f = \bar{x}_1\bar{x}_2 + x_1\bar{x}_3\bar{x}_4 + x_1\bar{x}_2\bar{x}_3 + x_2x_3x_4$$

Cost = 4 AND gates + 1 OR gate + (2 + 3 + 3 + 3 inputs to the AND gates + 4 inputs to the OR gate) = 20

The K-map for \bar{f} is

| | | \bar{x}_1 | | x_1 | |
|-------------|-------------|-------------|-------|-------------|-------|
| | | \bar{x}_2 | x_2 | \bar{x}_2 | x_2 |
| \bar{x}_3 | \bar{x}_4 | 0 | 1 | 0 | 0 |
| | x_4 | d | 1 + 1 | 1 | 0 |
| x_3 | x_4 | d | d | 0 | 1 |
| | \bar{x}_4 | 0 | d | 1 | 1 + 1 |

$$\begin{aligned}\bar{f} &= \bar{x}_1x_2 + x_2\bar{x}_3x_4 + x_1x_3\bar{x}_4 + x_1\bar{x}_2x_3. \quad (8) \\ \Rightarrow f &= (x_1 + \bar{x}_2)(\bar{x}_2 + x_3 + \bar{x}_4) \\ &\quad (\bar{x}_1 + \bar{x}_3 + x_4)(\bar{x}_1 + x_2 + \bar{x}_3). \quad (9)\end{aligned}$$

Cost = 4 OR gates + 1 AND gate + (2 + 3 + 3 + 3 inputs to OR gates and 4 inputs to the AND gate) = 20

Problem 9 Derive a minimum-cost realization of the four-variable function that is equal to 1 if

exactly two or exactly three of its variables are equal to 1; otherwise it is equal to 0. [1, Prob 2.46] [10 marks]

Solution

| Row | x_1 | x_2 | x_3 | x_4 | f | Reason |
|-----|-------|-------|-------|-------|---|---------------|
| 0 | 0 | 0 | 0 | 0 | 0 | |
| 1 | 0 | 0 | 0 | 1 | 0 | |
| 2 | 0 | 0 | 1 | 0 | 0 | |
| 3 | 0 | 0 | 1 | 1 | 1 | 2-var are one |
| 4 | 0 | 1 | 0 | 0 | 0 | |
| 5 | 0 | 1 | 0 | 1 | 1 | 2-var |
| 6 | 0 | 1 | 1 | 0 | 1 | 2-var |
| 7 | 0 | 1 | 1 | 1 | 1 | 3-var |
| 8 | 1 | 0 | 0 | 0 | 0 | |
| 9 | 1 | 0 | 0 | 1 | 1 | 2-var |
| 10 | 1 | 0 | 1 | 0 | 1 | 2-var |
| 11 | 1 | 0 | 1 | 1 | 1 | 3-var |
| 12 | 1 | 1 | 0 | 0 | 1 | 2-var |
| 13 | 1 | 1 | 0 | 1 | 1 | 3-var |
| 14 | 1 | 1 | 1 | 0 | 1 | 3-var |
| 15 | 1 | 1 | 1 | 1 | 0 | |

K-map for the function f is

| | | \bar{x}_1 | | x_1 | |
|-------------|-------------|-------------|-------|-------------|-------|
| | | \bar{x}_2 | x_2 | \bar{x}_2 | x_2 |
| \bar{x}_3 | \bar{x}_4 | 0 | 0 | 1 | 0 |
| | x_4 | 0 | 1 | 1 + 1 | 1 |
| x_3 | x_4 | 1 | 1 | 0 | 1 |
| | \bar{x}_4 | 0 | 1 | 1 + 1 | 1 |

$$\begin{aligned}f &= x_2\bar{x}_3x_4 + x_2x_3\bar{x}_4 + x_1\bar{x}_2x_4 + \bar{x}_1x_3x_4 \\ &\quad + x_1x_3\bar{x}_4 + x_1x_2\bar{x}_3\end{aligned}$$

Cost = 5 AND gates + 1 OR gate + (5*3 inputs per AND gate + 5 inputs to the OR gate) = 26

K-map for the inverted function \bar{f} is

| | | \bar{x}_1 | | x_1 | |
|-------------|-------------|---------------|-------|-------------|-------|
| | | \bar{x}_2 | x_2 | \bar{x}_2 | x_2 |
| \bar{x}_3 | \bar{x}_4 | 1 + 1 + 1 + 1 | 1 | 0 | 1 |
| | x_4 | 1 | 0 | 0 | 0 |
| x_3 | x_4 | 0 | 0 | 1 | 0 |
| | \bar{x}_4 | 1 | 0 | 0 | 0 |

$$\begin{aligned}\bar{f} &= \bar{x}_1\bar{x}_3\bar{x}_4 + \bar{x}_2\bar{x}_3\bar{x}_4 + \bar{x}_1\bar{x}_2\bar{x}_3 \\ &\quad + \bar{x}_1\bar{x}_2\bar{x}_4 + x_1x_2x_3x_4 \\ f &= (x_1 + x_3 + x_4)(x_2 + x_3 + x_4) \\ &\quad (x_1 + x_2 + x_3)(x_1 + x_2 + x_4) \\ &\quad (\bar{x}_1 + \bar{x}_2 + \bar{x}_3 + \bar{x}_4)\end{aligned}$$

| | | \bar{x}_1 | | | x_1 | | | |
|-------------|-------------|-------------|-------|-------------|-------------|-------|-------------|---|
| | | \bar{x}_2 | x_2 | | \bar{x}_2 | x_2 | | |
| | | \bar{x}_3 | x_3 | \bar{x}_3 | \bar{x}_3 | x_3 | \bar{x}_3 | |
| \bar{x}_4 | \bar{x}_5 | 1 | 1 | d | 1 | 1 | 0 | 1 |
| | x_5 | 1 | d | 1 | 1 | d | 1 | 0 |
| x_4 | x_5 | 1 | d | d | 1 | 1 | d | 0 |
| | \bar{x}_5 | 0 | 1 | 1 | 0 | 0 | 1 | 0 |

Table 2: K-map for f in problem 10. The essential minterm for the Essential Prime implicant is indicated with the same color.

| | | \bar{x}_1 | | | x_1 | | | |
|-------------|-------------|-------------|-------|-------------|-------------|-------|-------------|---|
| | | \bar{x}_2 | x_2 | | \bar{x}_2 | x_2 | | |
| | | \bar{x}_3 | x_3 | \bar{x}_3 | \bar{x}_3 | x_3 | \bar{x}_3 | |
| \bar{x}_4 | \bar{x}_5 | 0 | 0 | d | 0 | 0 | 0 | 1 |
| | x_5 | 0 | d | 0 | 0 | d | 0 | 1 |
| x_4 | x_5 | 0 | d | d | 0 | 0 | d | 1 |
| | \bar{x}_5 | 1 | 0 | 0 | 1 | 1 | 0 | 1 |

Table 3: 5-var K-map for \bar{f} in problem 10. The essential minterms for Essential Prime Implicants (EPI) is shown in the same color.

Cost = 5 OR gates + 1 AND gate + (4 * 3 inputs per OR gate + 4 inputs to one OR gate + 5 inputs to 1 AND gate = 27

The minimal cost representation is the SOP representation:

$$f = x_2\bar{x}_3x_4 + x_2x_3\bar{x}_4 + x_1\bar{x}_2x_4 + \bar{x}_1x_3x_4 + x_1x_3\bar{x}_4 + x_1x_2\bar{x}_3$$

Problem 10 Find the minimum-cost SOP and POS forms for the function $f(x_1, \dots, x_5) = \sum m(0, 1, 3, 4, 6, 8, 9, 11, 13, 14, 16, 19, 20, 21, 22, 24, 25) + D(5, 7, 12, 15, 17, 23)$. [1, Prob 2.42] [10 marks]

Solution

The K-map for the function is in Table 2.

$$f = \bar{x}_1x_5 + \bar{x}_1x_3 + x_2x_3 + \bar{x}_3\bar{x}_4 + \bar{x}_2x_5$$

Cost = 5 AND gates + 1 OR gate + (5*2 inputs per AND gate + 5 inputs to one OR gate) = 21

The K-map for the function inverse is given in Table 3

$$\begin{aligned} \bar{f} &= x_1x_2x_3 + \bar{x}_3x_4\bar{x}_5 + x_1x_2x_4 \\ \implies f &= (\bar{x}_1 + \bar{x}_2 + \bar{x}_3)(x_3 + \bar{x}_4 + x_5) \\ &\quad (\bar{x}_1 + \bar{x}_2 + \bar{x}_4) \end{aligned}$$

Cost = 3 OR gate + 1 AND gate + (3*3 inputs to the OR gates and 3 inputs to the AND gate)=16.

References

- [1] S. Brown and Z. Vranesic. *Fundamentals of Digital Logic with Verilog Design: Third Edition*. McGraw-Hill Higher Education, 2013.

| | | x_1 | | | | | | $x_1 = 0/1$ | | | | | | | |
|-------------|-------------|-------------|-------|-------------|-------------|-------|-------------|-------------|-------------|-------------|-------------|-------------|------|-------|-------|
| | | \bar{x}_2 | | | x_2 | | | \bar{x}_2 | | | x_2 | | | | |
| | | \bar{x}_3 | x_3 | \bar{x}_3 | \bar{x}_3 | x_3 | \bar{x}_3 | x_3 | \bar{x}_3 | \bar{x}_3 | x_3 | \bar{x}_3 | | | |
| \bar{x}_4 | \bar{x}_5 | 0 | 4 | 12 | 8 | 16 | 20 | 28 | 24 | \bar{x}_4 | \bar{x}_5 | 0/16 | 4/20 | 12/28 | 8/24 |
| | x_5 | 1 | 5 | 13 | 9 | 17 | 21 | 29 | 25 | | x_5 | 1/17 | 5/21 | 13/29 | 9/25 |
| | x_5 | 3 | 7 | 15 | 11 | 19 | 23 | 31 | 27 | x_4 | x_5 | 3/19 | 7/23 | 15/31 | 11/27 |
| x_4 | \bar{x}_5 | 2 | 6 | 14 | 10 | 18 | 22 | 30 | 26 | | \bar{x}_5 | 2/18 | 6/22 | 14/30 | 10/26 |

Table 4: K-map for 5-variables with numbered minterms