

# ECE275 Project progress report (Due Nov 30th)

Instructor: Vikas Dhiman

November 22, 2022

## 1 VGA module

Watch the tutorial below and replicate it on the Altera FPGA board,

- VGA Video Tutorial (Must be logged in to you Umaine account to view) : [Video Tutorial](#). There is a mistake in the video when instantiating the make\_box module, it should be `make_box make_first_player_paddle(` and not `module make_first_player make_box(`
- Example simple top level : [VGA\\_top.v](#)
- DE0 VGA Driver Module : [DE0\\_VGA.v](#)
- PLL (Phase Locked Loop) Verilog File : [PLL\\_PIXEL\\_CLK.v](#)
- QSF File : [VGA\\_top.qsf](#)


Required submissions for project progress report on Nov 30 before class.

1. A working version of `VGA_top.v` and `VGA_top.qsf` that can draw a box on the screen.

## 2 Breaking application into smaller parts

### 2.1 Slow clock

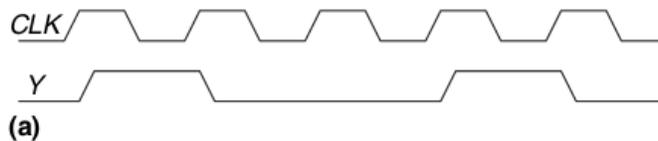**Problem 1.** A divide-by- $N$  counter has one output and no inputs. The output  $Y$  is HIGH for one clock cycle out of every  $N$ . In other words, the output divides the frequency of the clock by  $N$ . The waveform for a divide-by-3 counter is shown here:



Sketch circuit designs for such a counter



```

`timescale 10ms/1ms
module testbouncingball ();
  reg clock;
  reg reset;
  reg [9:0] paddle_y;
  initial begin
    clock = 0;
    paddle_y = 10'd240;
    #5 reset = 1;
    #15 reset = 0;
  end
  end
  always #5 clock = ~clock;

  wire [9:0] ballx;
  wire [9:0] bally;

  bouncingball bball( clock , reset , paddle_y , ballx , bally );
endmodule

```

Figure 1: Sample testbouncingball.sv

### 3. Screenshot of the waveform generated using ModelSim.

## 2.3 Moving paddle


**Problem 5.** Design a circuit for 1 pixel paddle on a 4x4 pixel screen. Assume that it can take two inputs from *BUTTONs*, one for moving up and another one for moving down. You can design this circuit by hand (Why)?

**Problem 6.** Design the above circuit using Verilog.

**Problem 7.** Once you have the VGA example working, extend the above problem to 640x480 resolution with you

Required submissions for project progress report on Nov 30 before class.

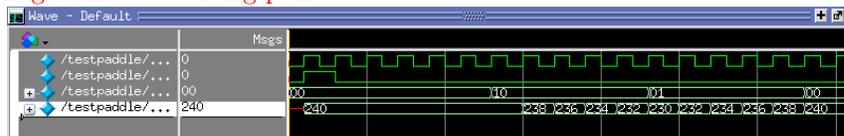1. A paddle.sv that takes 2 bit input up\_down for up button and down button and outputs the Y-coordinate of the paddle which moves according to the button pressed.
2. A testpaddle.sv that runs at 50Hz and shows the paddle\_y to increase and decreases witch change in up and down input. You may use the code from Figure 2 as a starting point.



```

`timescale 10ms/1ms
module testpaddle();
    reg clock;
    reg reset;
    reg [1:0] up_down; // up down buttons
    wire [9:0] paddle_y; // y coordinate of paddle y
    initial begin
        clock = 0;
        reset = 0;
        up_down = 2'b00;
        #1 reset = 1;
        #2 reset = 0;
        #10 up_down = 2'b10; // after delay of 100ms press up
        #10 up_down = 2'b01; // after delay of 100ms press down
        #10 up_down = 2'b00; // after delay of 100ms release both
    end
    always #1 clock = ~clock; // 20ms clock time period

    paddle pd1( clock , reset , up_down , paddle_y);
endmodule

```

Figure 2: Sample testpaddle.sv

### 3. Screenshot of the waveform generated using ModelSim.

## 2.4 Ball paddle collision

**Problem 8.** *Combine the bouncing ball problem with the moving paddle problem and bounce the ball only if the ball is about to hit the paddle, otherwise game is over. If the ball hits the paddle increment a score counter by 1.*