

Sequential logic design

Vikas Dhiman for ECE275


December 5, 2022

1 Objectives


1. Design combinational circuits using multiplexers and decoders

2 Design combinational circuit using multiplexers [1, Section 2.8.1] 2.8.2


2.1 Review: 2to1 Multiplexer (MUX)

 

S	D ₁	D ₀	Y
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

 


$$Y = \bar{S}D_0 + SD_1$$

 

 2.2 Wider multiplexers

Draw the symbol for a 4:1 MUX, an 8:1 MUX and a $2^N : 1$ MUX and write corresponding Boolean expressions.



$S_1 S_0$
 $00 \Rightarrow Y = D_0$
 $01 \Rightarrow Y = D_1$

S ₁	S ₀	Y
0	0	D ₀
0	1	D ₁
1	0	D ₂
1	1	D ₃

$$\begin{aligned}
 Y = & \bar{S}_1 \bar{S}_0 D_0 \\
 & + \bar{S}_1 S_0 D_1 \\
 & + S_1 \bar{S}_0 D_2 \\
 & + S_1 S_0 D_3
 \end{aligned}$$

Only 1 minterm
can be true
at a time.

The minterm that
is true, selects
the data line

Minterms: $\bar{S}_1 \bar{S}_0, \bar{S}_1 S_0, S_1 \bar{S}_0, S_1 S_0$


Only 1 minterm can be true at a time.

The minterm that is true, selects the corresponding data line.

8:1 MUX


Draw a symbol, write an expression and TT

How many select lines?

 


$$\begin{aligned}
 Y = & \bar{S}_2 \bar{S}_1 \bar{S}_0 D_0 \\
 & + \bar{S}_2 \bar{S}_1 S_0 D_1 \\
 & + \bar{S}_2 S_1 \bar{S}_0 D_2 \\
 & \vdots \\
 & + S_2 S_1 S_0 D_7
 \end{aligned}$$

S_2	S_1	S_0	Y
0	0	0	D_0
0	0	1	D_1
0	1	0	D_2
	⋮		
1	1	1	D_7

 


3-input

 

Easy

Example 1. Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 8:1 MUX.

A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

 

when $ABC = 011$
then
 $Y = D_3 = 1$

Remark 1. A $2^N : 1$ MUX can be used to program any N -input logic function.

Example 2. Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 4:1 MUX and NOT gates only.

① Design which input should go to the SELECT inputs
and " " " " " " " DATA inputs


Remark 2. A $2^{N-1} : 1$ MUX can be used to program any N -input logic function, if we use literals on the input side.

Example 3. Design a circuit for $Y = \bar{A}C + \bar{A}B + B\bar{D}$ using a 8:1 MUX and NOT gates only. Also design using 4:1 MUX and other gates. fewest gates.

3 Encoders and Decoders

Example 4. Draw the symbol and the truth table for 2:4 decoder. Also write the logic expressions.

 Example 5. Draw the symbol and the truth table for 3:8 decoder, 4:16 decoder and $N : 2^N$ decoder. Also write the logic expressions.





$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$

The input signals that occur in most implicants go to the select bits.


B must connect to the select sign

because B occurs 3 times in the implicants while A and C occur 2 times.

AB goes to SELECT signals

  

BC select

 


when $BC = 00$

when $BC = 01$
 $Y = 1$
 $Y = A$

A	Y
0	0
1	1

 
$$Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$$



when $B = 11$

A	Y
0	1
1	0

$Y = \bar{A}$

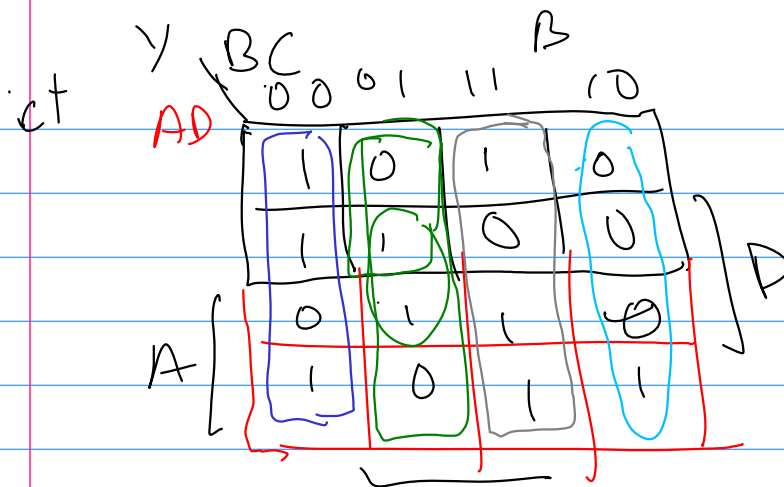

when $BC = 00$

$$Y = f(A, D) = ?$$

$$Y = \bar{A} + \bar{D}$$

when $BC = 01$




$$Y = D$$

when $BC = 11$


$$Y = A + \bar{D}$$

when $BC = 10$

$$Y = A\bar{D}$$

   

- $D_0 = \bar{A} + \bar{D}$
- $D_1 = D$
- $D_2 = A + \bar{D}$
- $D_3 = A\bar{D}$

 

Example 6. *Design a circuit for a XOR gate using a 2:4 decoder and an OR gate.*

Example 7. *Design a circuit for $Y = A\bar{B} + \bar{B}\bar{C} + \bar{A}BC$ using a 3:8 decoder and an OR gate.*

3.1 Encoders

Example 8. *Draw symbol and truth table for a 4:2 priority encoder.*

Example 9. *Draw symbol and truth table for a 8:3 priority encoder.*

References

- [1] Sarah L Harris and David Harris. *Digital design and computer architecture*. Morgan Kaufmann, 2022.